

# RF and Microwave Amplifier Power Added Efficiency, Fact and Fiction

Dr. Dominic FitzPatrick

Principal Consultant, PowerRFul Microwave

[www.powerful-microwave.co.uk](http://www.powerful-microwave.co.uk)



A National  
Instruments  
Company™



**AWR Corporation – A National Instruments Company**

[www.awrcorp.com](http://www.awrcorp.com)

## The Innovation Leader in High-Frequency EDA

### Product Portfolio:


- Microwave Office™ - MMIC, RF PCB and module
- Visual System Simulator™ - Wireless comms/radar
- AXIEM® - 3D planar EM
- Analyst™ - 3D finite element method (FEM) EM
- Analog Office® - RFIC

### Global Presence (direct offices)

- Los Angeles, California (headquarters)
- California, Wisconsin, Colorado
- United Kingdom and Finland
- Japan, Korea and China

## RF and Microwave Design Software

- MMIC
- RF PCB
- Modules

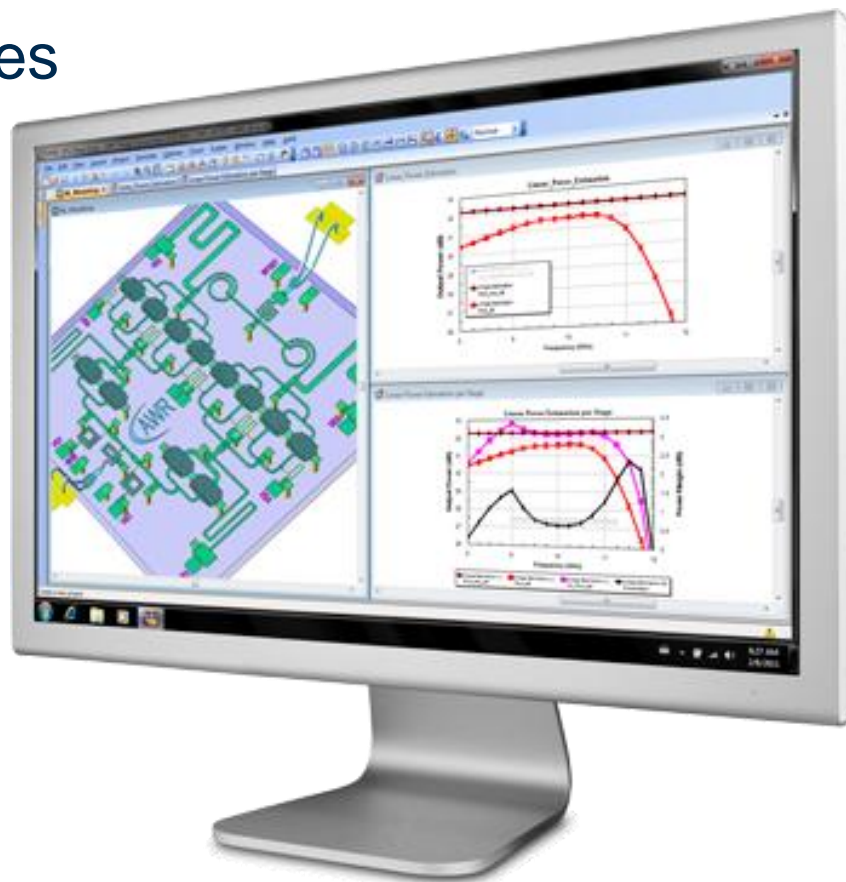

**Amplifier Technology Uses Microwave Office to Design High Performance Amplifiers While Cutting 50% Off Their Design Time**

"Microwave Office has helped us characterize appropriate parameters for each prototype design, evaluate possible variants and simulate the device performance straight from the design stage. In my experience Microwave Office is the best design solution available on the market."

Paul Deacon  
Senior RF Design Engineer  
Amplifier Technology







- Innovative Technology:
  - APLAC - Harmonic Balance
  - ACE - Circuit Extraction
  - AXIEM - Electromagnetics
- Flexible & Friendly Environment
  - Microsoft look-n-feel UI
  - Design concurrency
  - Plug-n-play sockets
    - ICED for DRC/LVS
    - EM for many
- Foundry Support: III/V PDKs
  - CREE, GCS, Northrop Grumman
  - OMMIC, RFMD, UMS
  - WIN & TriQuint




Photograph of the NDPA MMIC.

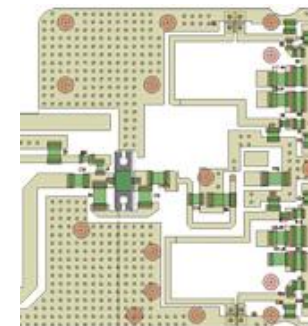

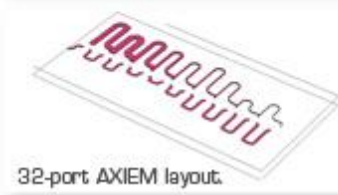Microwave Office layout of the driver board for the 20MHz - 520MHz, 125W power amplifier.



32-port AXIEM layout.

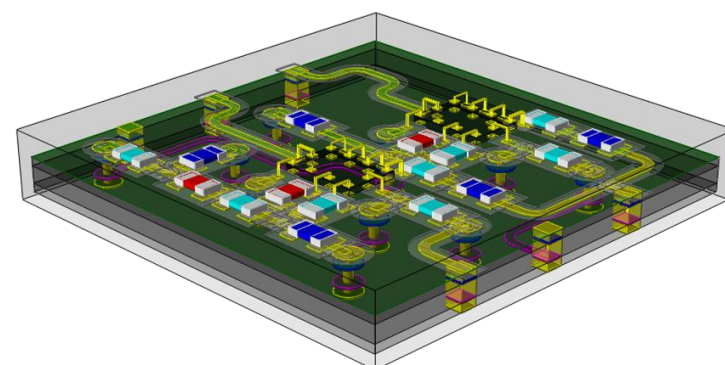

# Learn More...

## Online:

- [www.awrcorp.com](http://www.awrcorp.com)
- AWR.TV

## Communities:

- Facebook
- Twitter
- LinkedIn
- YouTube

## Email:

- [info@awrcorp.com](mailto:info@awrcorp.com)



# Cree: *the World's Largest Pure Play WBG Company*



## Overview


- Founded in 1987
- Public since 1993 (Nasdaq: CREE)
- Headquartered in Durham, NC
- Strong patent portfolio

## Global Reach

- 12 major locations
- 6000 employees
- Fiscal 2013 Revenues \$1.4B


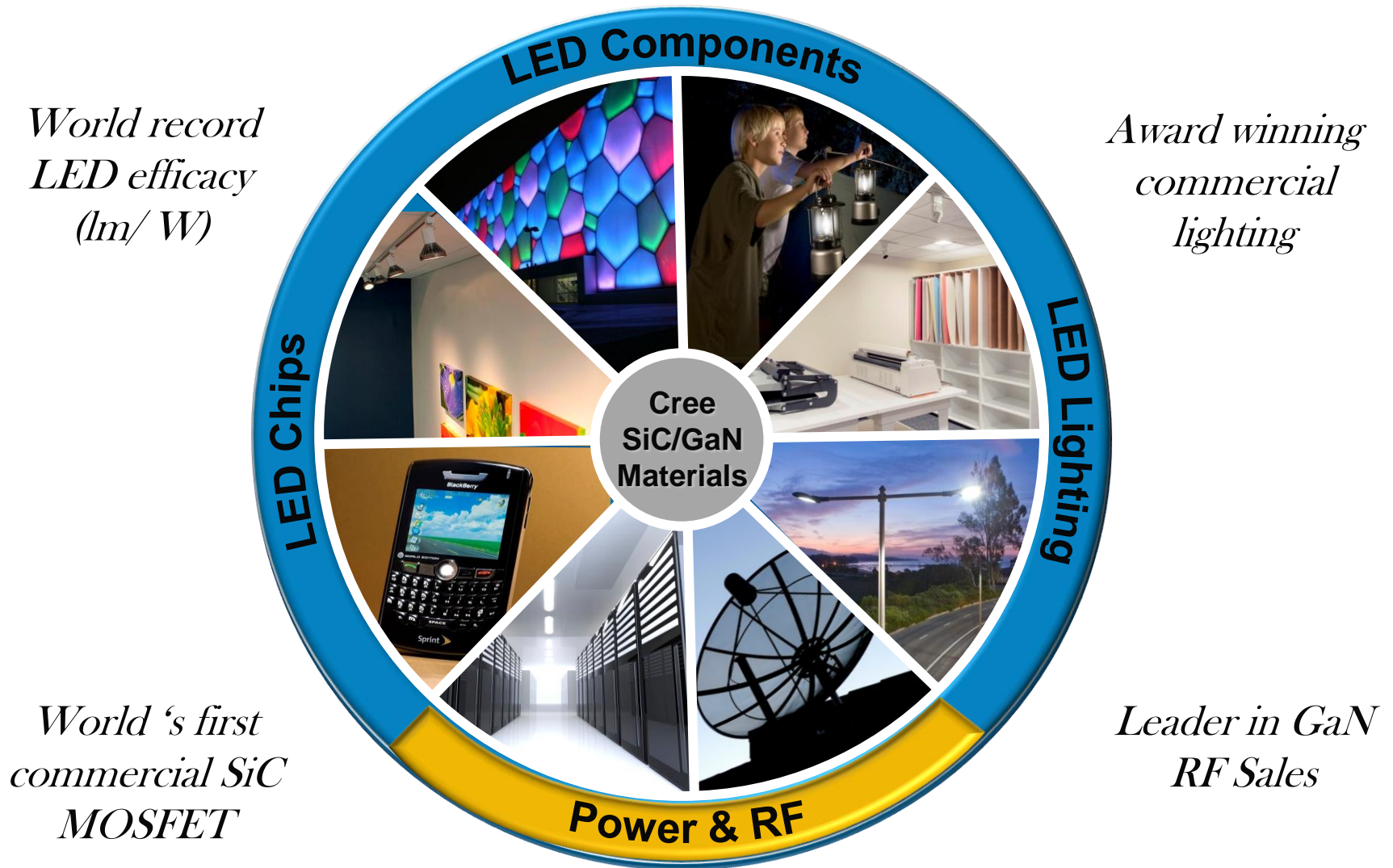
# Cree businesses – a leading player in each sector






# Cree WBG Center of Excellence for Power and RF



## Cree economies of scale

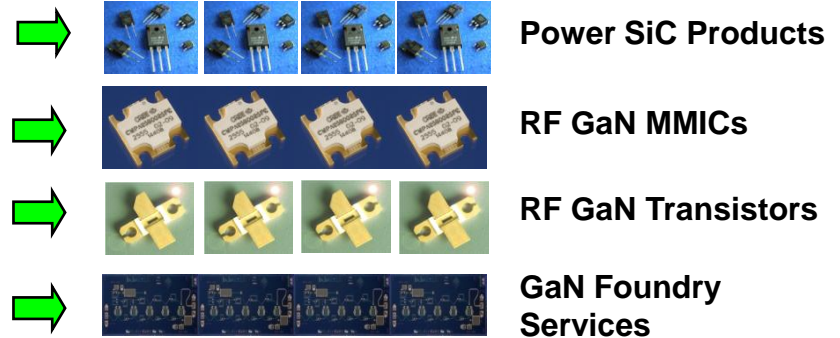

- Opened August 2006
- SiC and GaN RF and Power products
- World's largest dedicated WBG production device facility
  - Shared high volume Power and RF lines
  - Benefits from LED commercial infrastructure for volume SiC wafer and GaN epi supply
    - Billions of LEDs produced yearly
- Providing rapid cost reduction to industry **"economies of scale"**



# RF and Microwave Amplifier Power Added Efficiency, Fact and Fiction



Dr. Dominic FitzPatrick  
Principal Consultant,  
PowerRFul Microwave

[www.powerful-microwave.co.uk](http://www.powerful-microwave.co.uk)

# Power Added Efficiency – The Basics

$$PAE = \frac{(RFP_{OUT} - RFP_{IN})}{DCP_{IN}} \%$$

Why is it important?

- *Smaller power supply, less current drawn*
  - *Smaller, lighter DC supply cables*
- *Less heat generated*
  - *Cooler running, higher reliability*
  - *Lower weight,*
  - *The higher the performance.*



But, it doesn't come for free; and it becomes harder to improve the efficiency the higher we go, i.e. 10% increase from 30-40% ✓  
from 60-70% 😞 from 70-80% 😞

# Power Added Efficiency – The Basics

$$PAE = \frac{(RFP_{OUT} - RFP_{IN})}{DCP_{IN}} \%$$

What does the equation mean?

- ❖ *Note:-  $RFP_{IN}$  means 'IN' to the device, not the source power, i.e. better input match higher PAE?*
- ❖ *Higher gain, higher PAE – GaN advantage!*


Don't get confused with Drain Efficiency.

$$DE = \frac{RFP_{OUT}}{DCP_{IN}} \%$$

Is DE actually a useful measure without including the impact of gain?




# Input & PAE

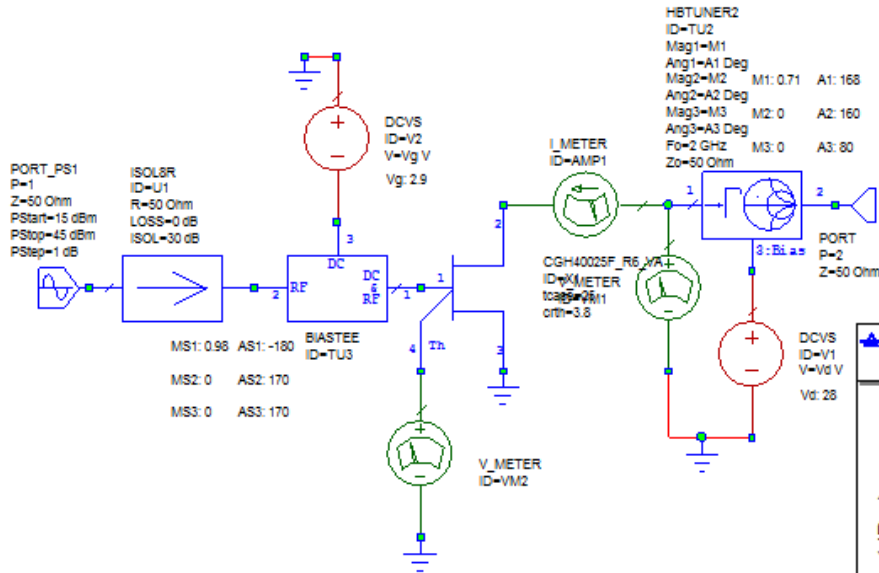


$$PAE = \frac{(RFP_{OUT} - RFP_{IN})}{DCP_{IN}} \%$$

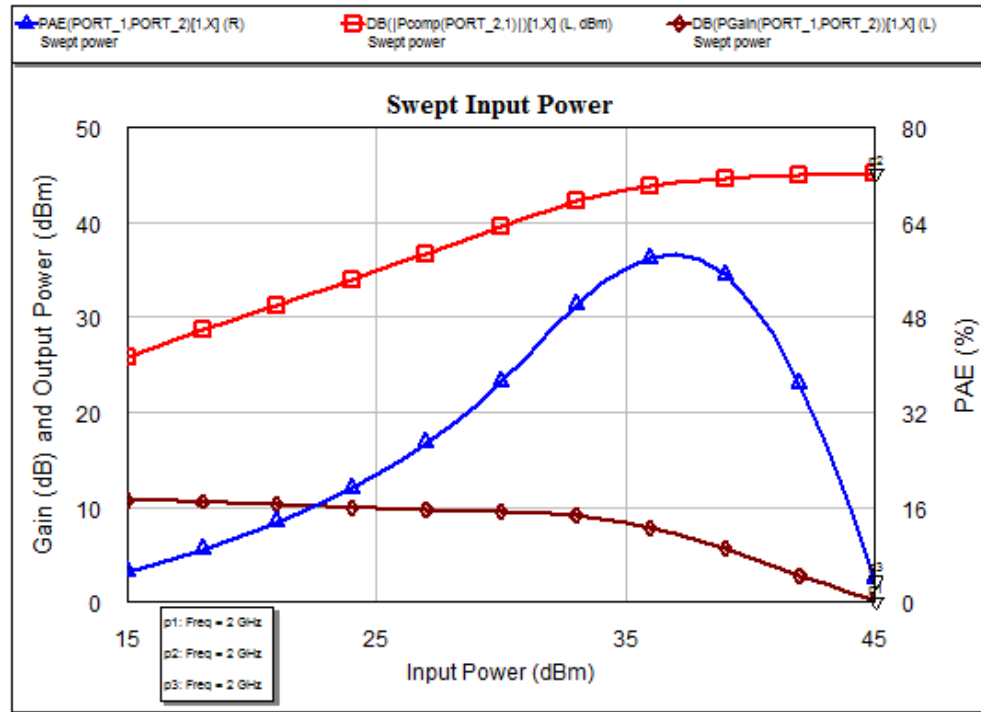With the isolator no power is reflected back and so  $RFP_{IN} = \text{source power}$ .  
Higher  $RFP_{IN}$  lower PAE




# Input & PAE

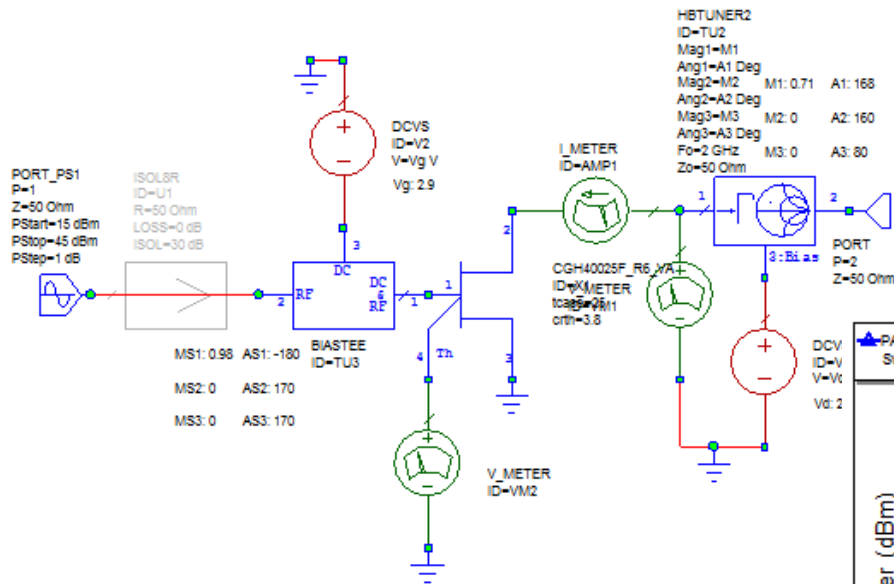


$$PAE = \frac{(RFP_{OUT} - RFP_{IN})}{DCP_{IN}} \%$$

Without the isolator the power reflected by the device is subtracted from source power to give  $RFP_{IN}$ .

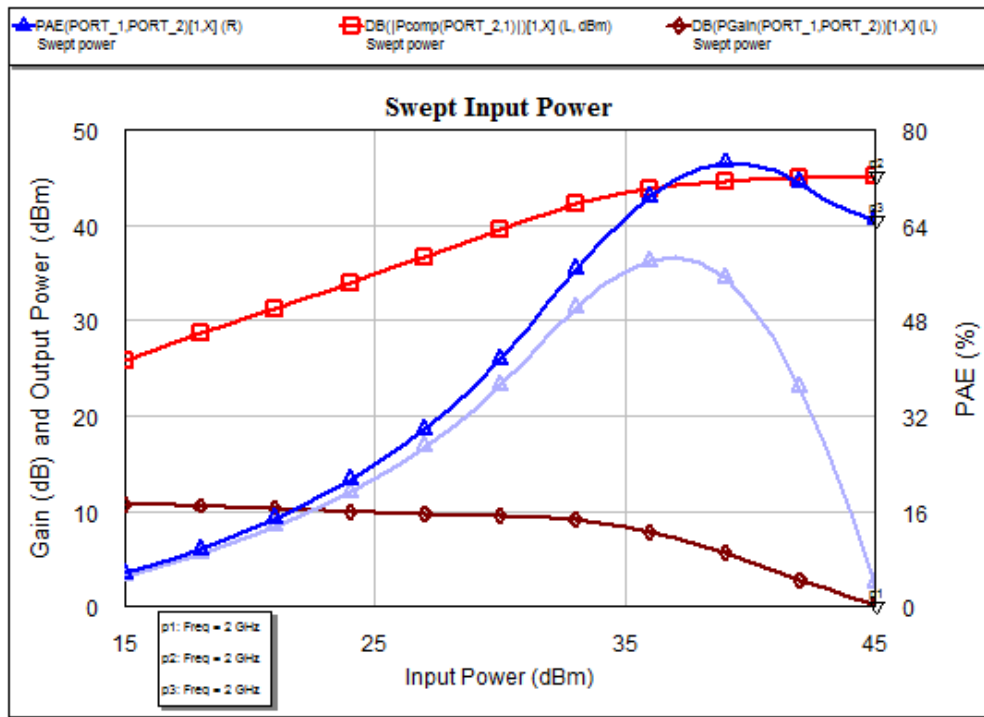With the isolator no power is reflected back and so  $RFP_{IN} = \text{source power}$ .  
Higher  $RFP_{IN}$  lower PAE




# Power Transfer


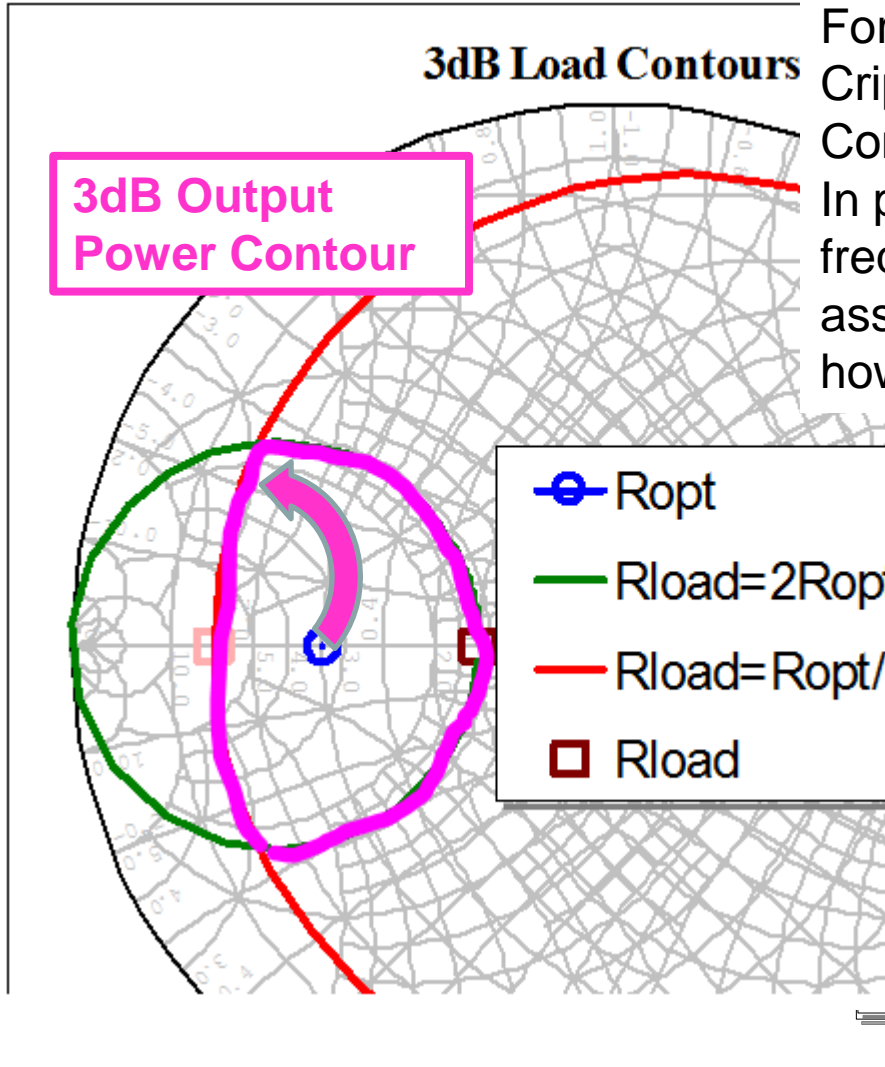


For mathematical proof of the contours see Cripps, "RF Power Amplifiers for Wireless Communications".

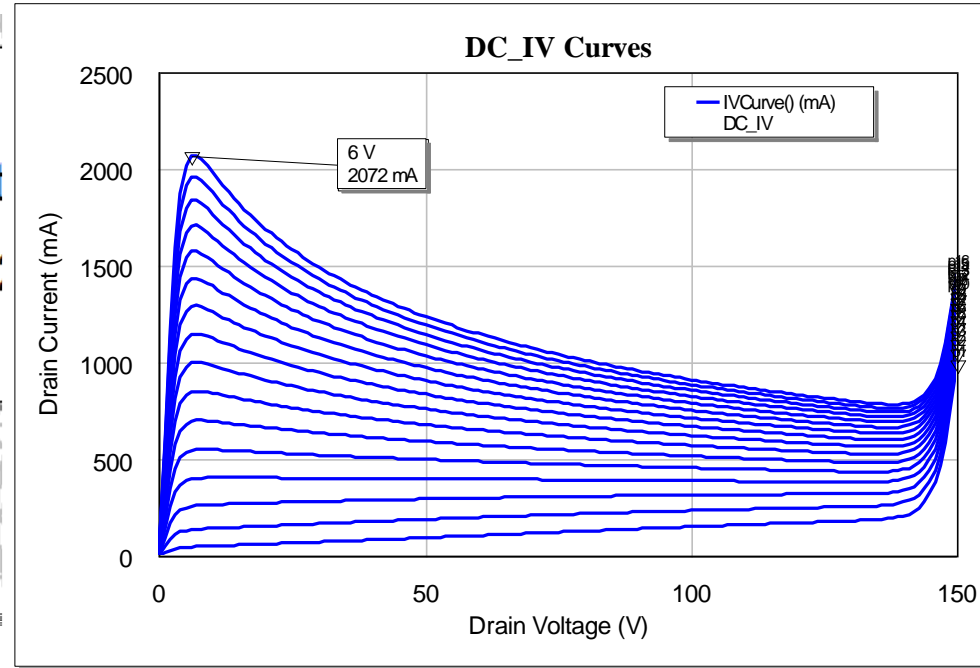In practice this would be tedious to do for every frequency, bias setting, drive level, etc. Also it assumes ideal DC-IV Curves in practice however:




# Power Transfer with a Nonlinear Model

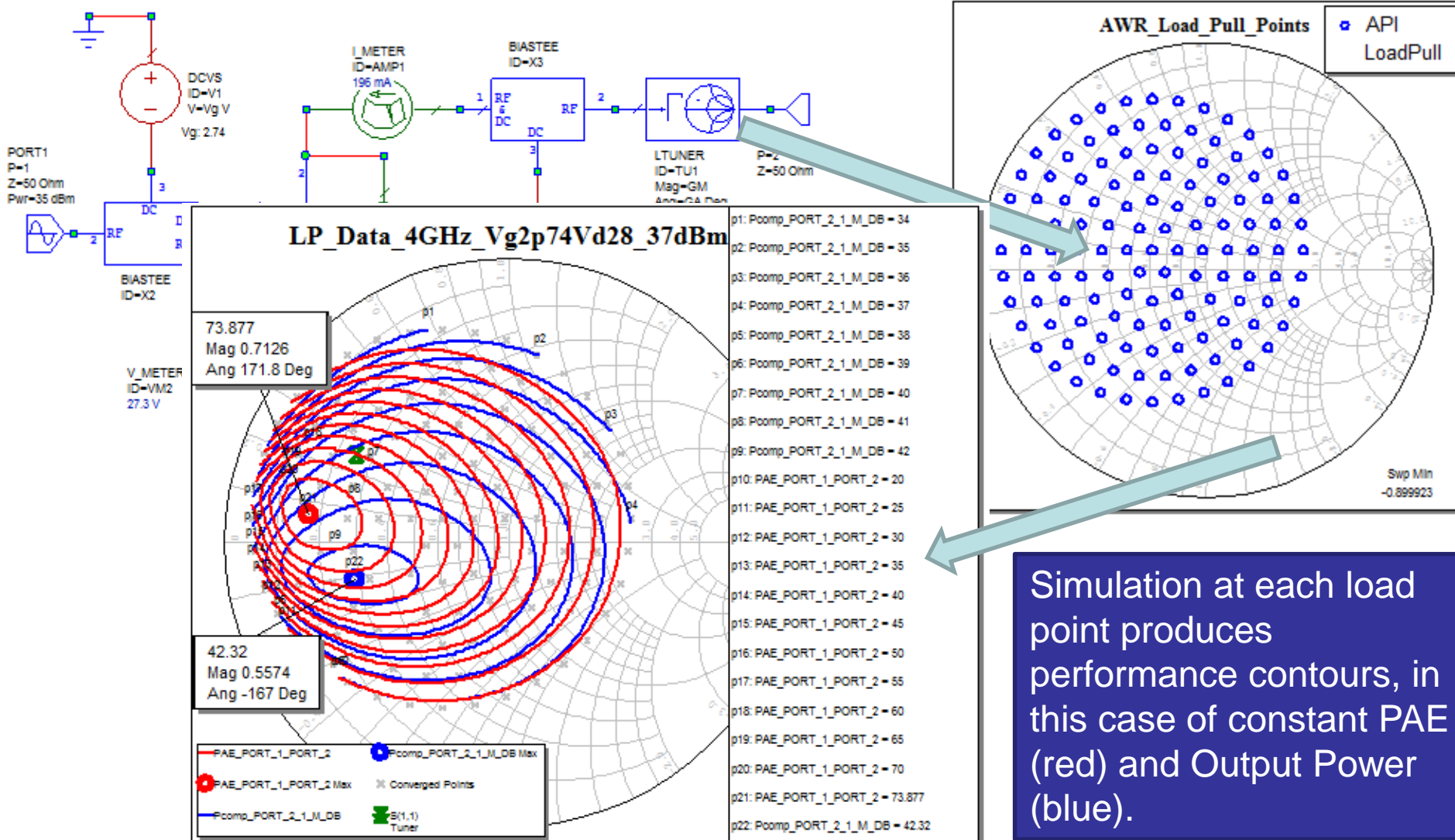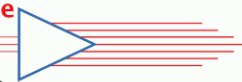

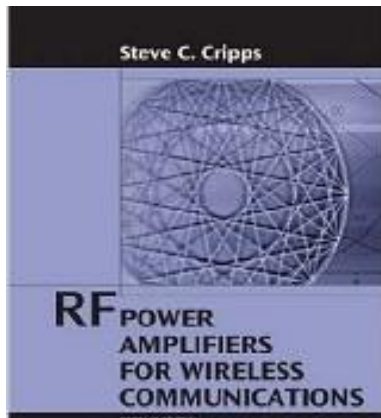Simulation at each load point produces performance contours, in this case of constant PAE (red) and Output Power (blue).








Not going to cover the theory of different classes of operation here

→ Already comprehensively covered such as by Prof. Steve Cripps.

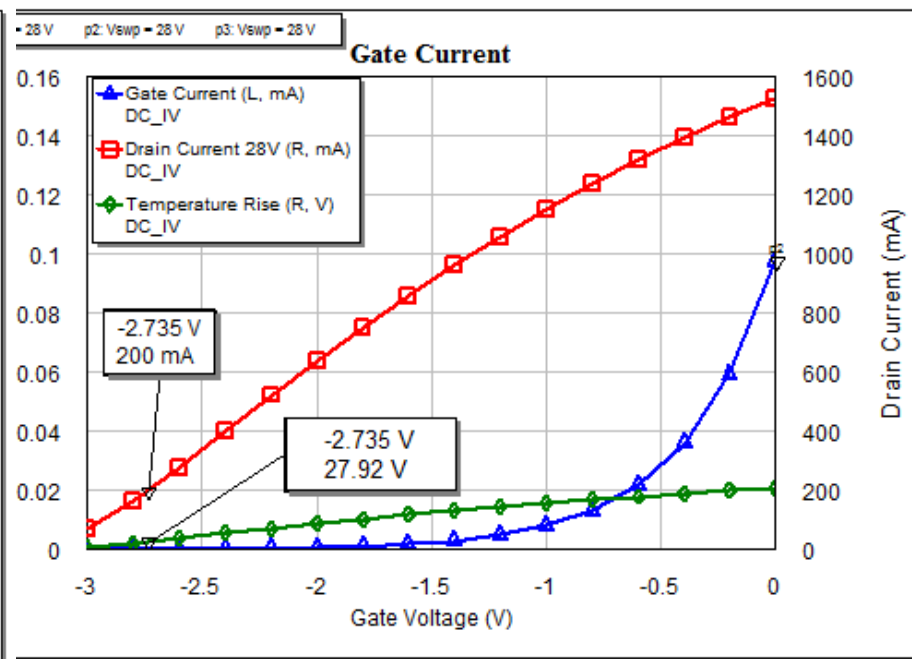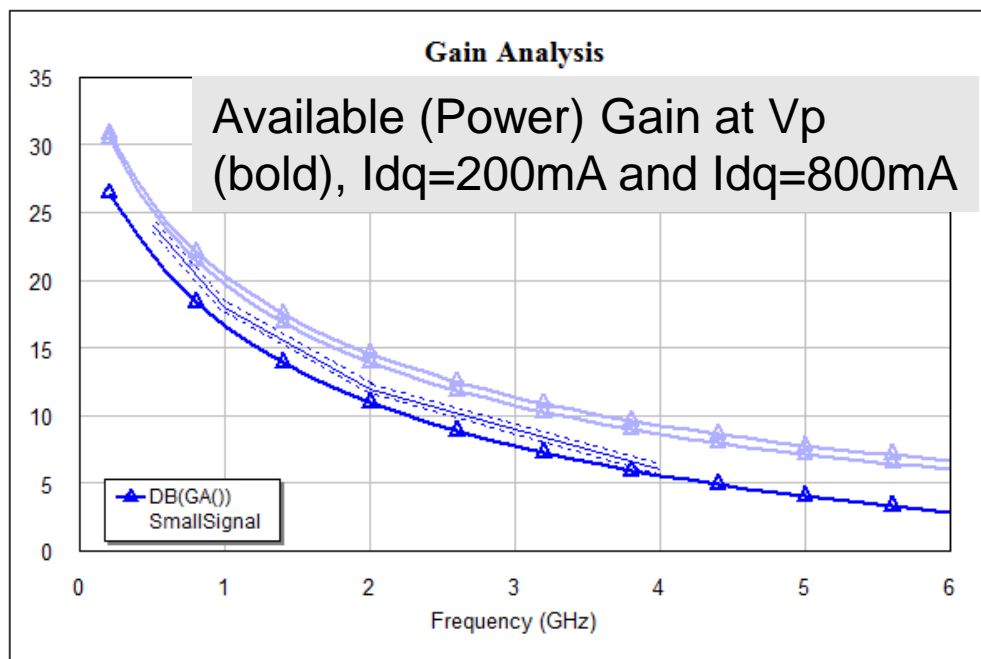But we will look at the effects of bias and remember that it is another variable open to use.




# Bias

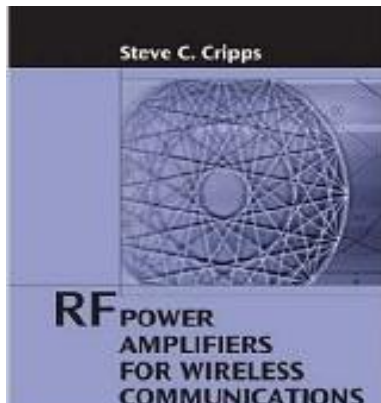


Not going to cover the theory of different classes of operation here

→ Already comprehensively covered such as by Prof. Steve Cripps.

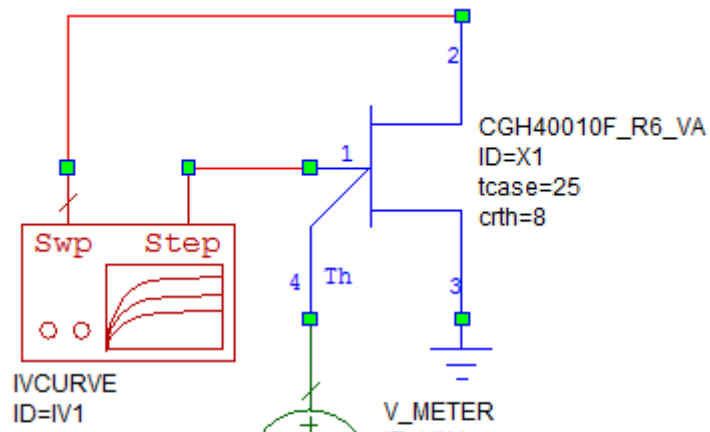But we will look at the effects of bias and remember that it is another variable open to use.




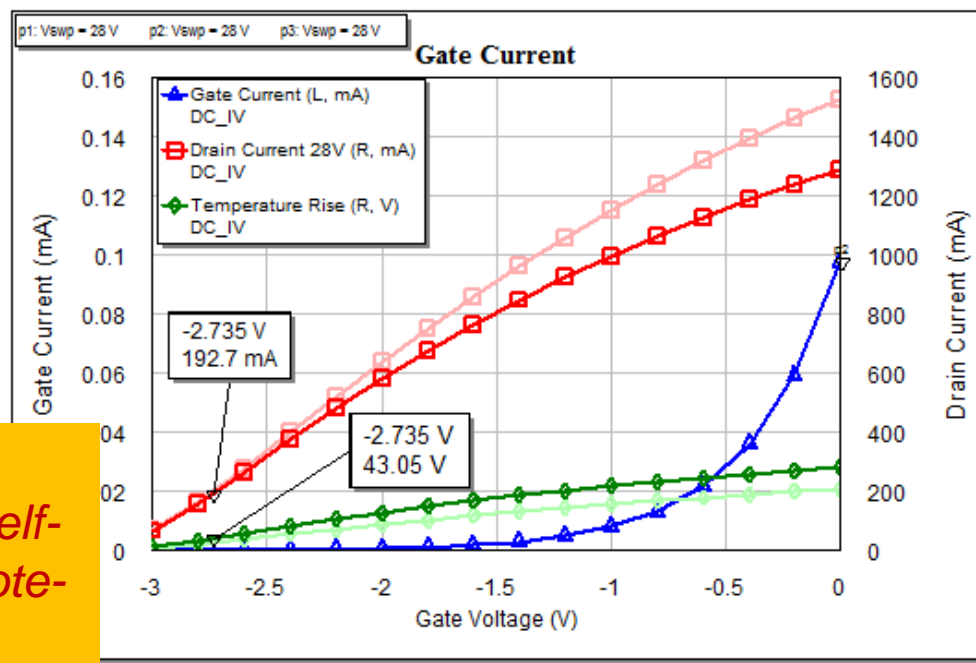
*Thermal Optimization of GaN HEMT Transistor Power Amplifiers Using New Self-heating Large Signal Model, Cree-App-Note-006*



# Tuners – Be Wary

LTUNER – Nice and simple, but what impedance does it present at other frequencies?




LTUNER – All frequencies are terminated with the same load impedance, in this case  $|GM| / \angle_{GA}^\circ$ .

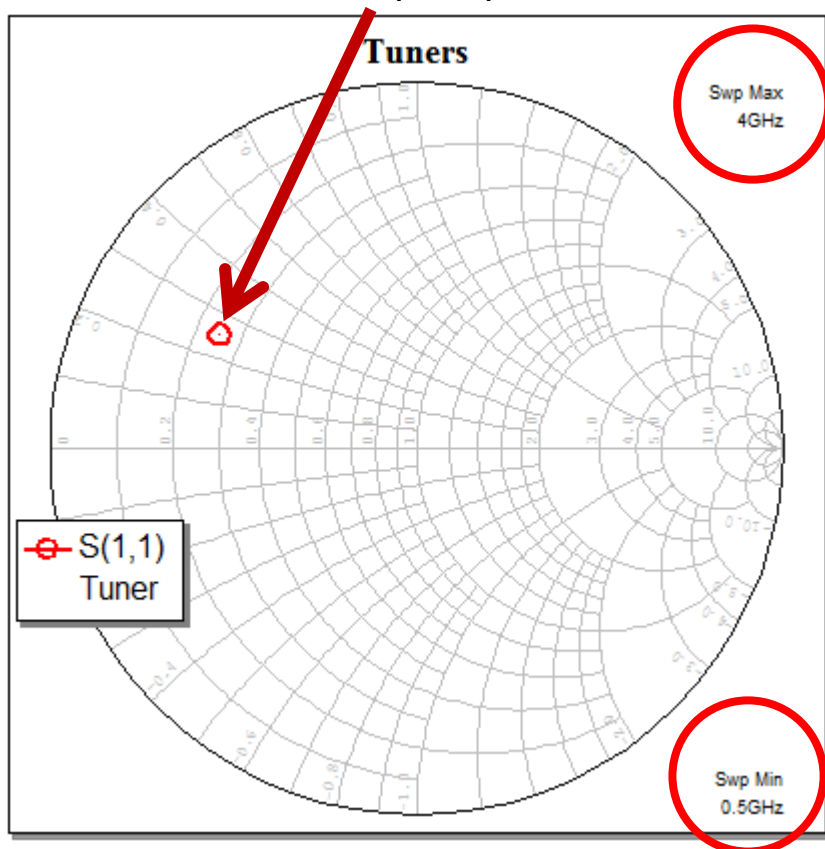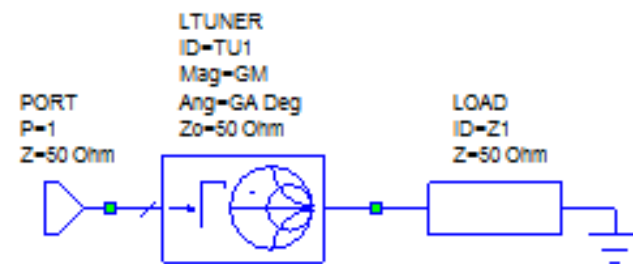
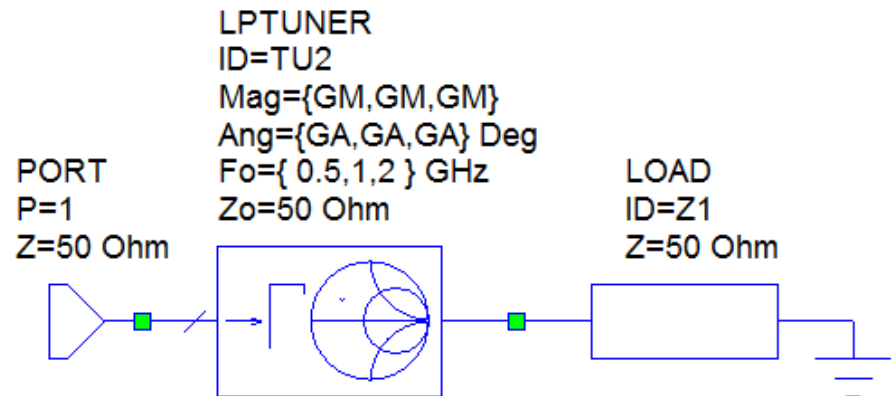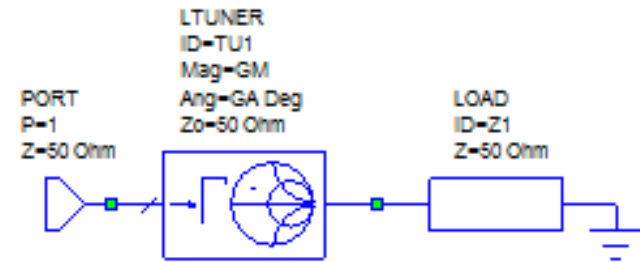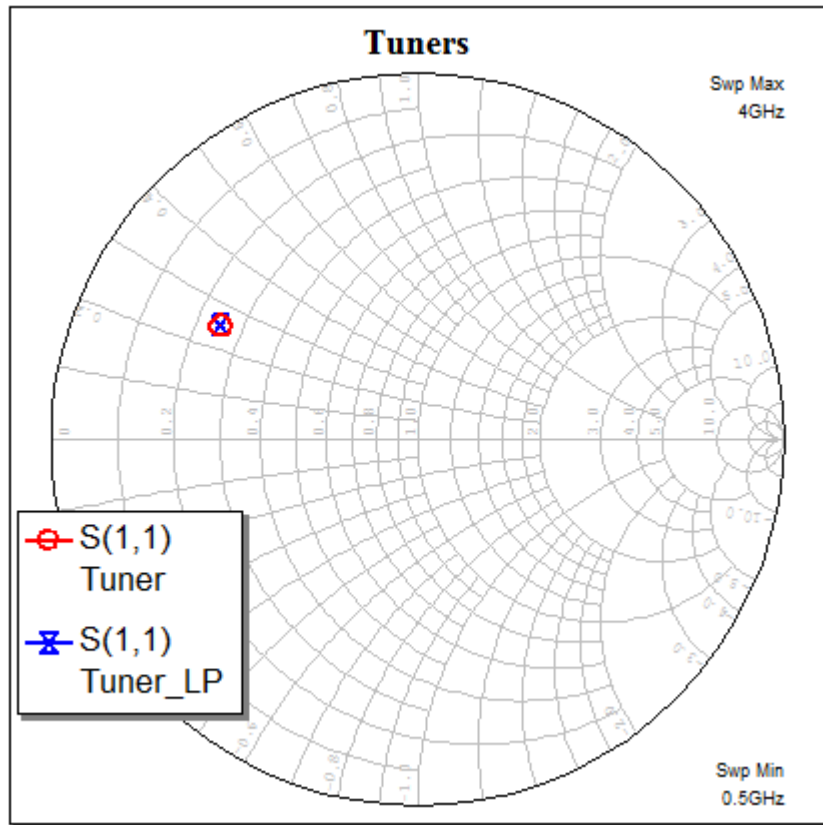
# Tuners – Be Wary

LTUNER – Nice and simple, but what impedance does it present at other frequencies?

LPTUNER – Define frequencies and their terminations, but if you don't define them they default.






Here we have defined 0.5, 1 & 2GHz but the other frequencies 2.5, 3, 3.5 and 4GHz also have defaulted to this load.


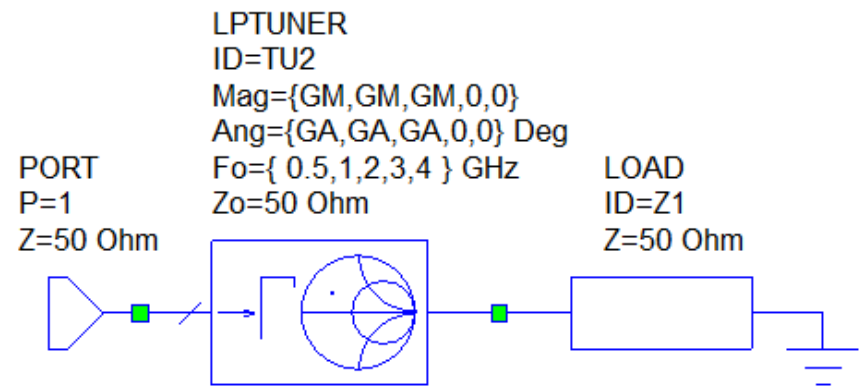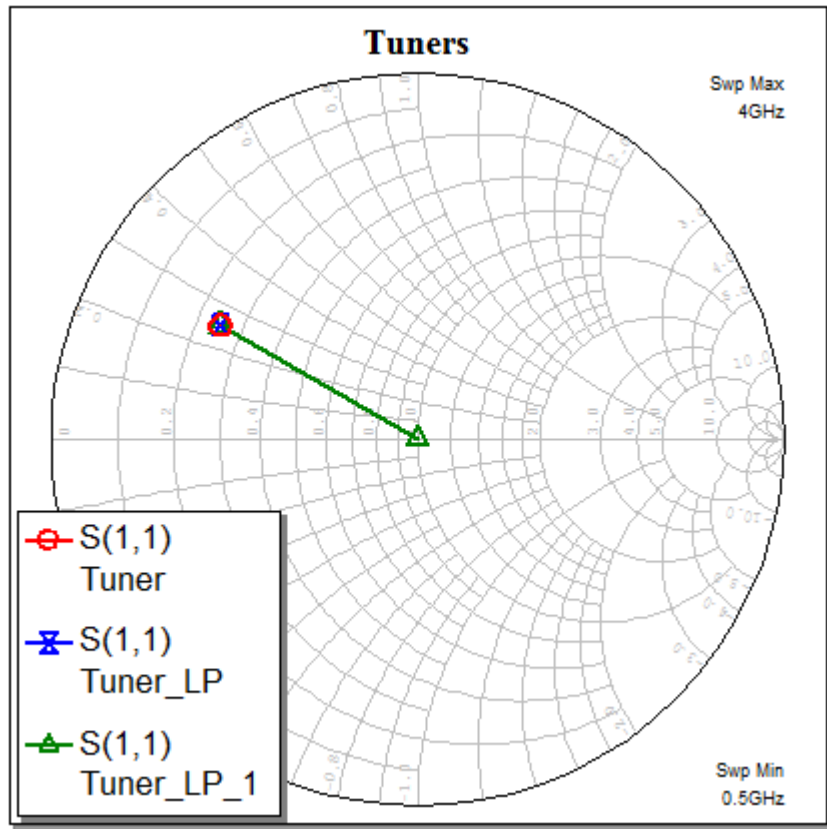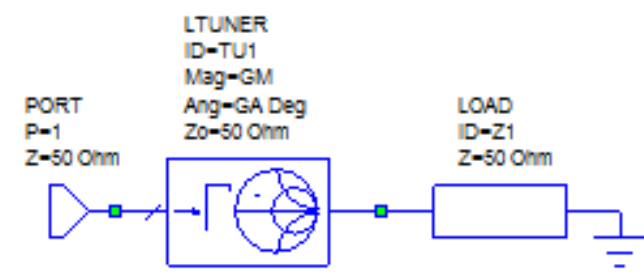
# Tuners – Be Wary

LTUNER – Nice and simple, but what impedance does it present at other frequencies?

LPTUNER – Define frequencies and their terminations, but if you don't define them they default.





Now we have defined different impedances to some of the frequencies, 3 & 4GHz are terminated in 50Ω

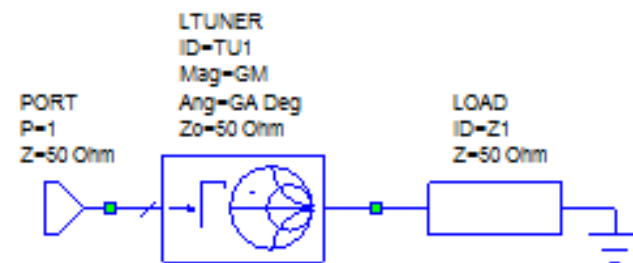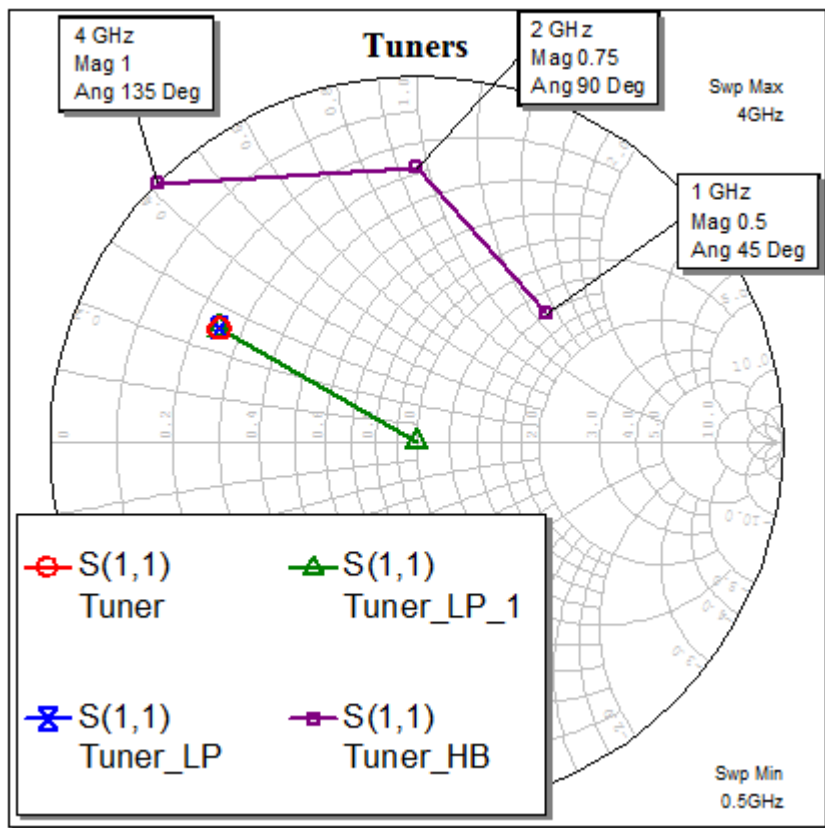
# Tuners – Be Wary

LTUNER – Nice and simple, but what impedance does it present at other frequencies?

HBTUNER – Takes care of the harmonic frequencies for you.



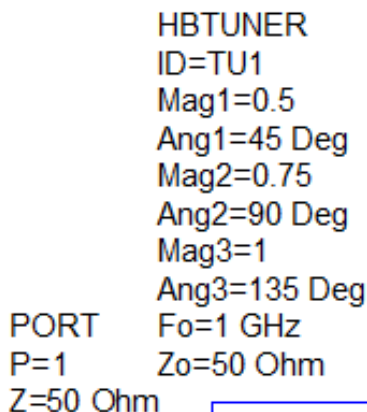
Takes care of the harmonic terminations of the defined frequency.




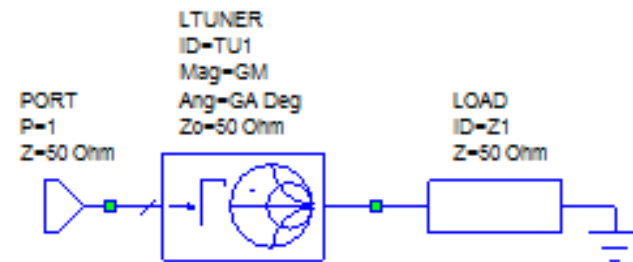
# Tuners – Be Wary

LTUNER – Nice and simple, but what impedance does it present at other frequencies?

HBTUNER – But.... Be aware of what happens at other frequencies and their terminations.




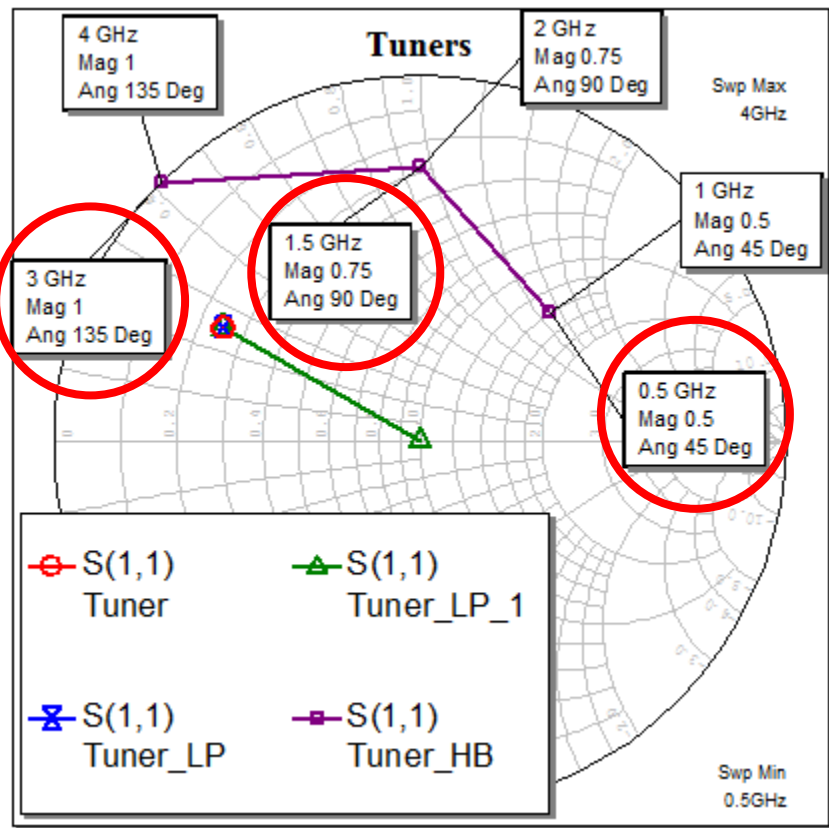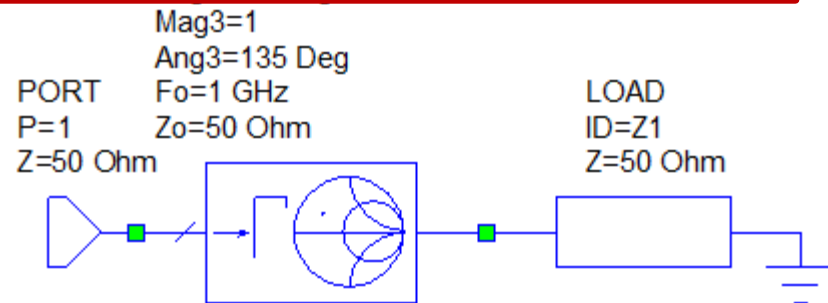**Harmonic impedance has an impact on device performance, so know where you have put yours!**




# Load Pull Set Up
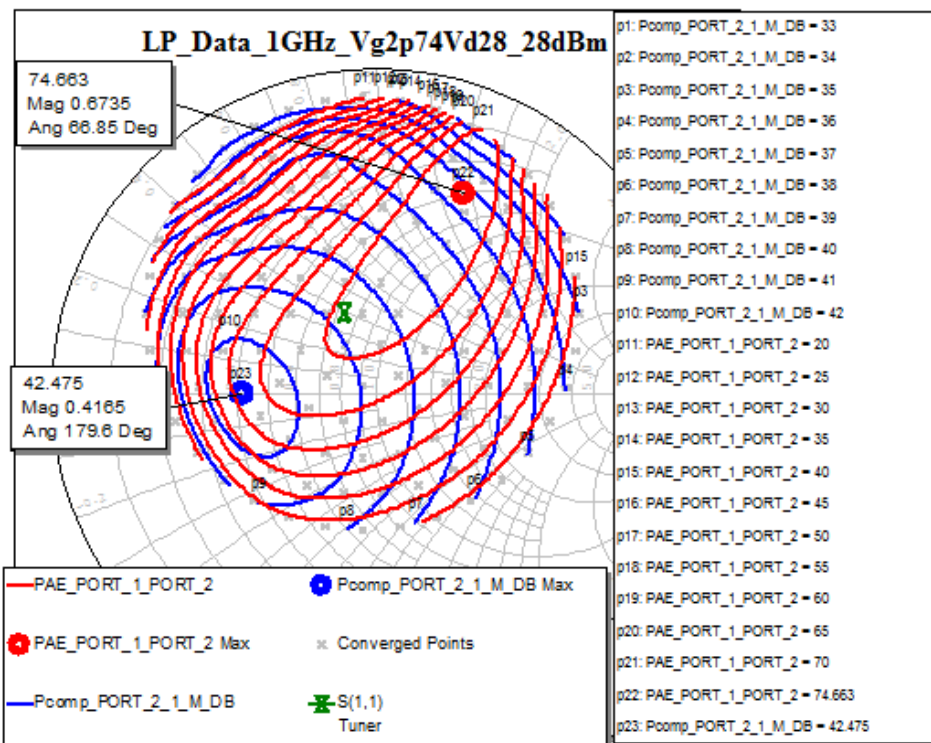
## Difference between using LTUNER and HBTUNER with harmonics terminated in 50Ω.



Load Pull with LTUNER

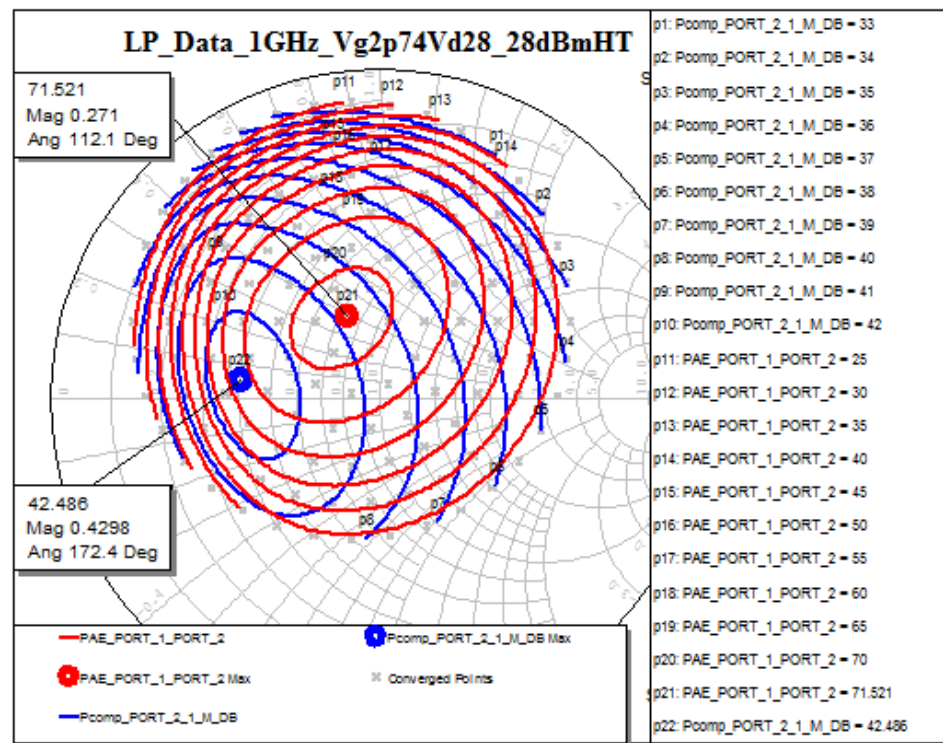


Load Pull with HBTUNER

Small impact on Pout – Significant on PAE

We use Load Pull so that we can visualise the trade-offs between parameters, typically PAE and Pout.

## Load Pull Check List

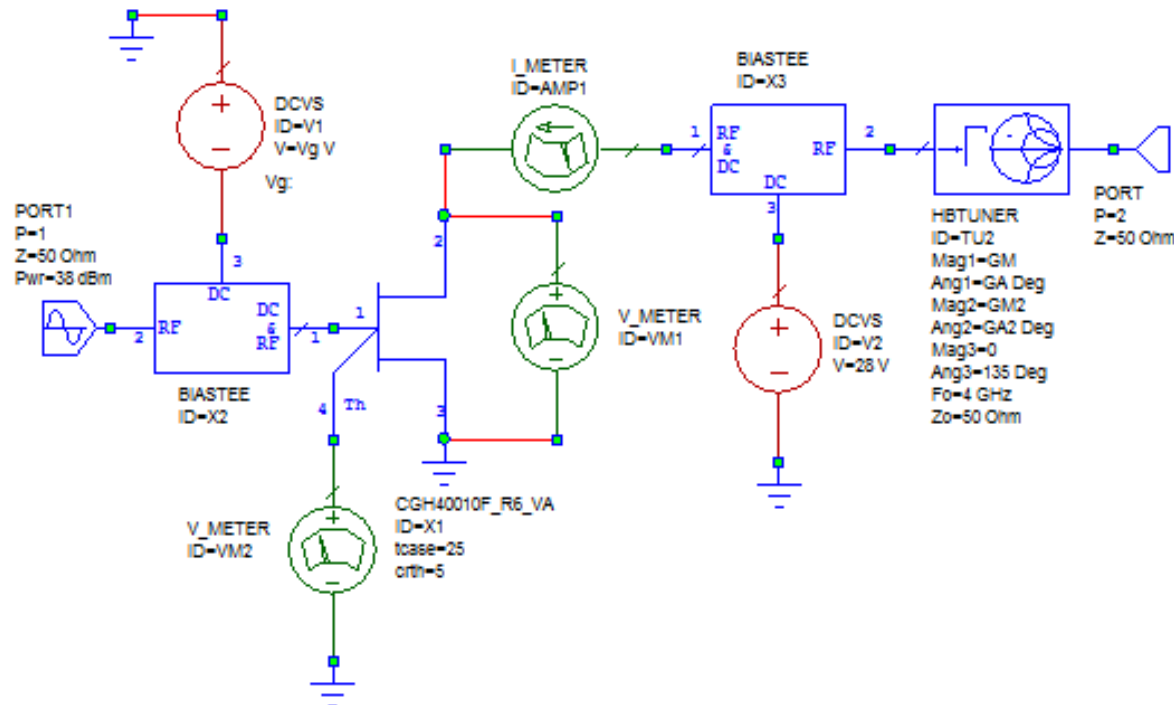1. Harmonic terminations – use HBTUNER for accurate/consistent results.
2. Input Power level, check that you are using the optimum drive level by conducting a power sweep.
3. Bias/Class of operation.





# Input Match Effects

Why does the input match change?



1. Intrinsic capacitance
2. Channel resistance
3. Load match

$$\Gamma_{IN} = S_{11} - \frac{S_{12}S_{21}\Gamma_L}{S_{22}\Gamma_L - 1}$$





*Intrinsic Cree GaN HEMT Models allow more accurate waveform engineered PA designs*

Ray Pengelly and Bill Pribble, Cree RF Products



ARMMS, April, 2013

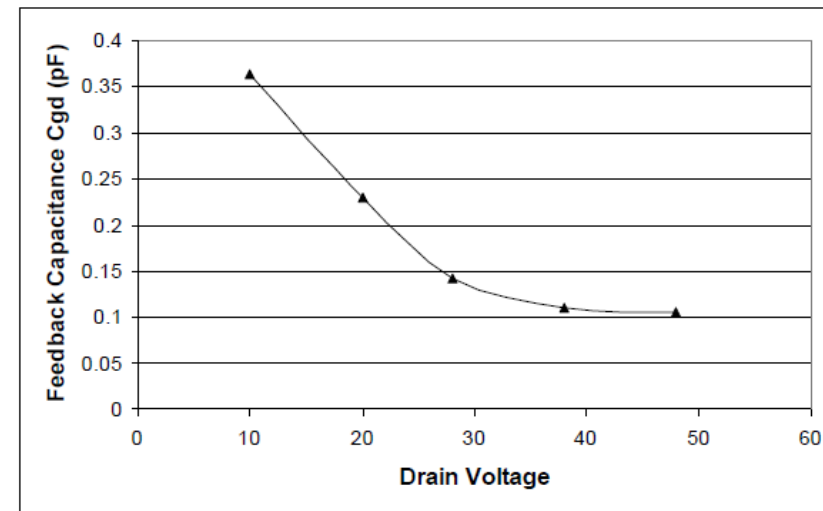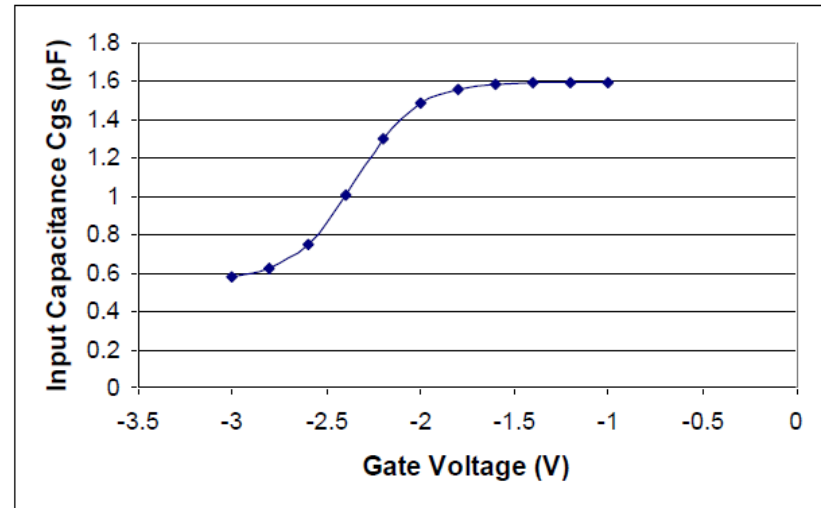

# Effect of Load on Input Match

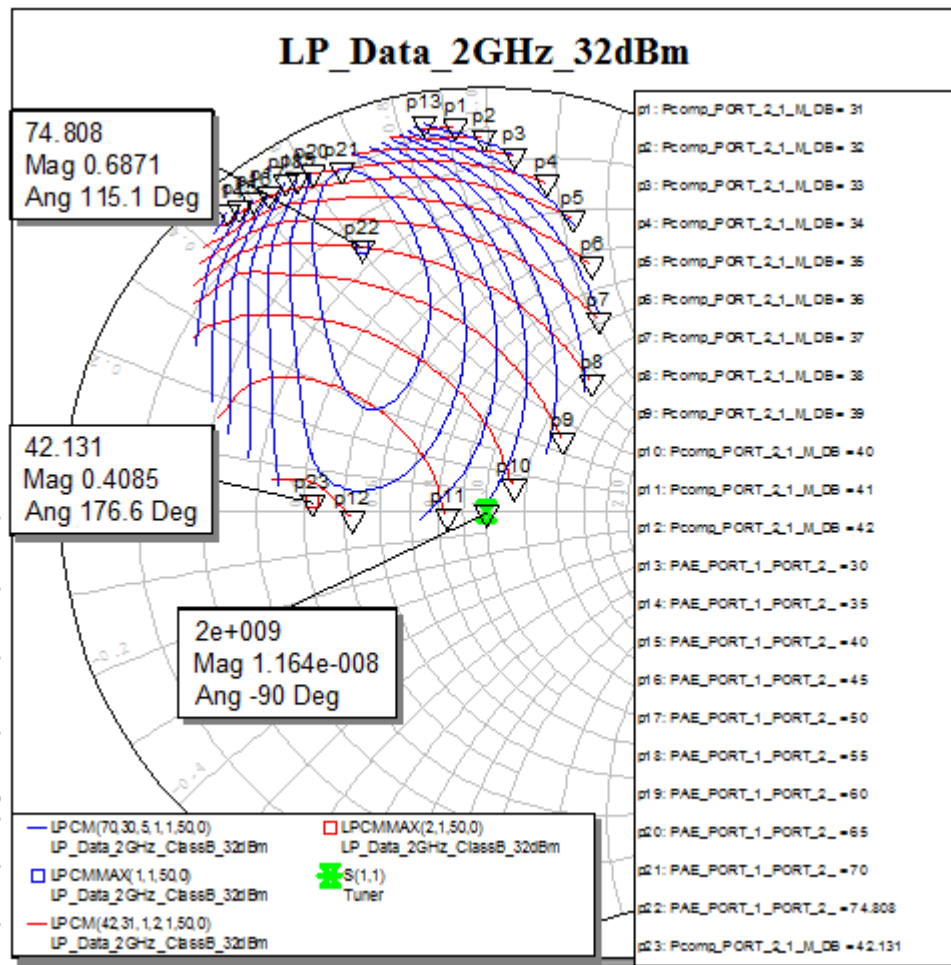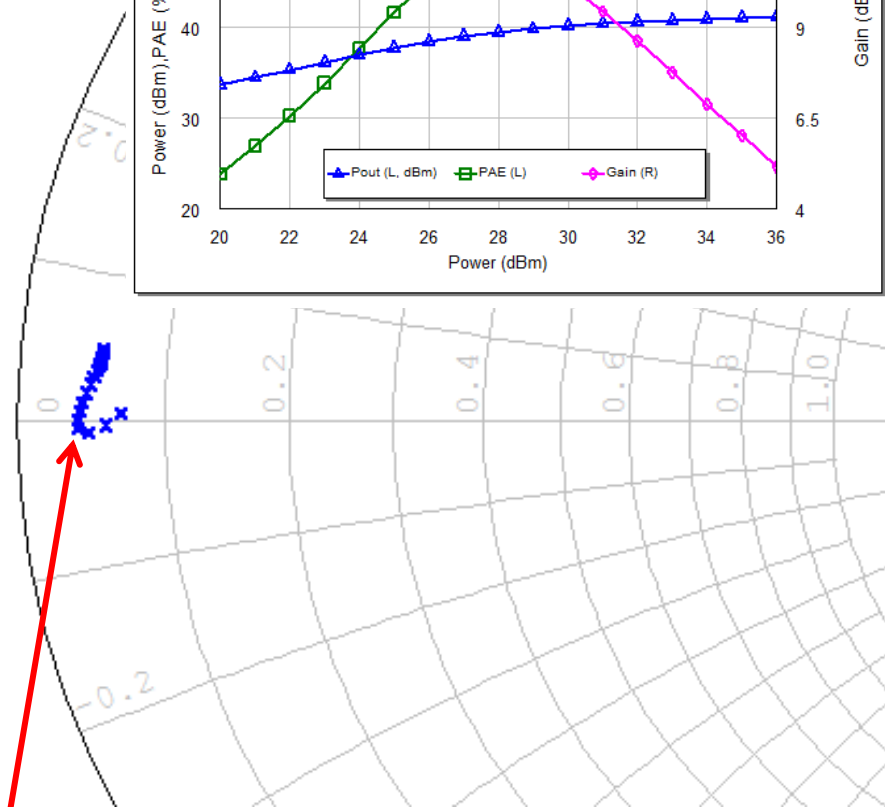
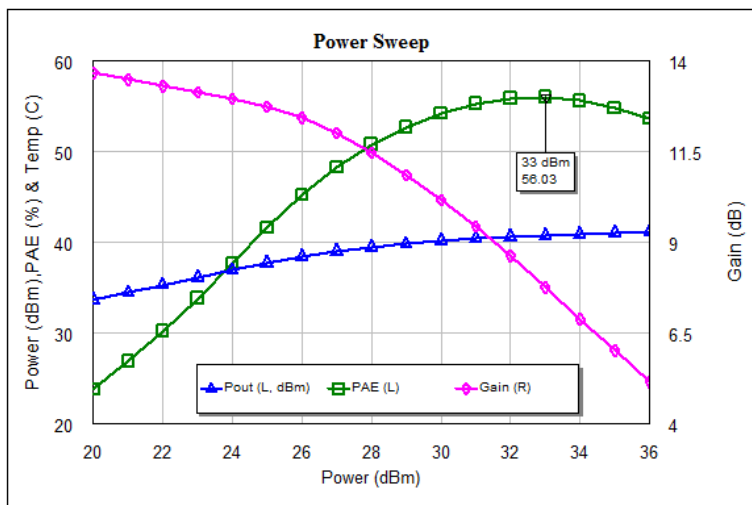
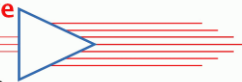


# Effect of Load on Input Match

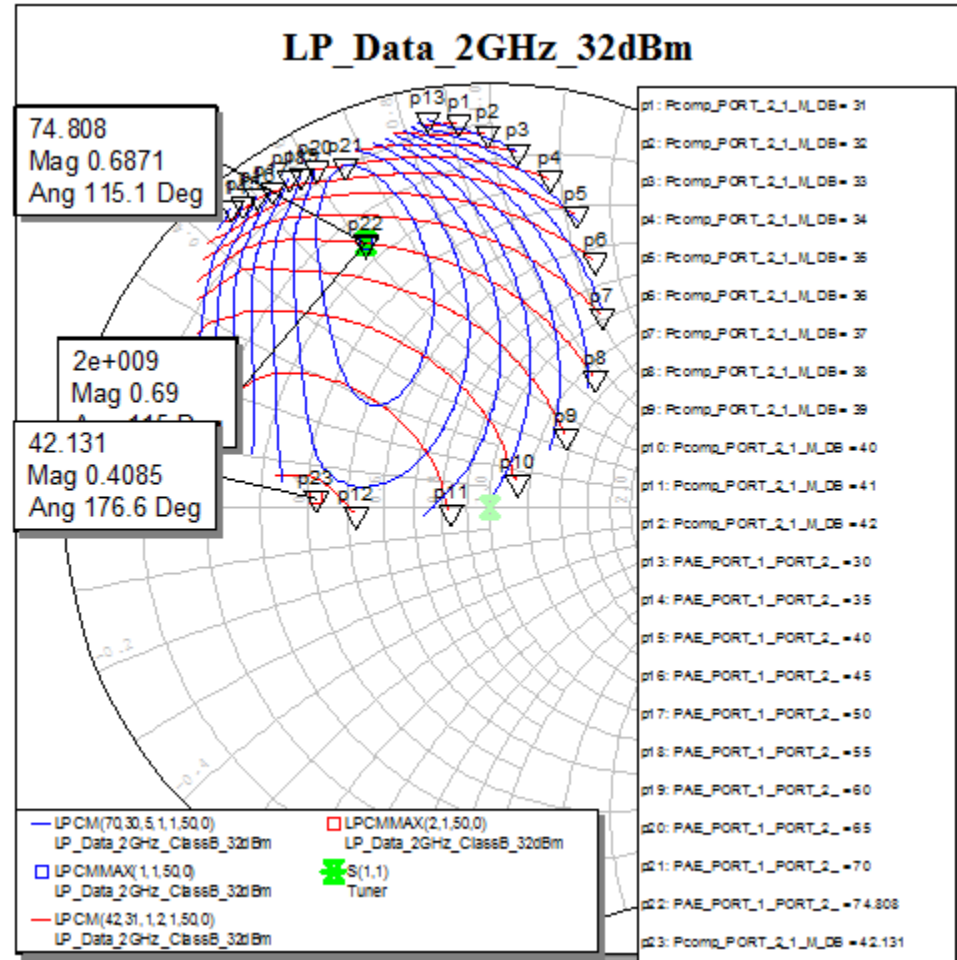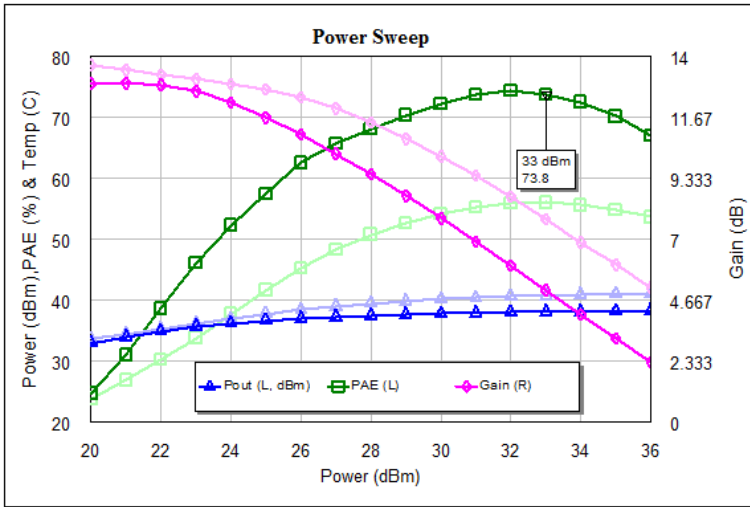

33dBm

# Effect of Load on Input Match

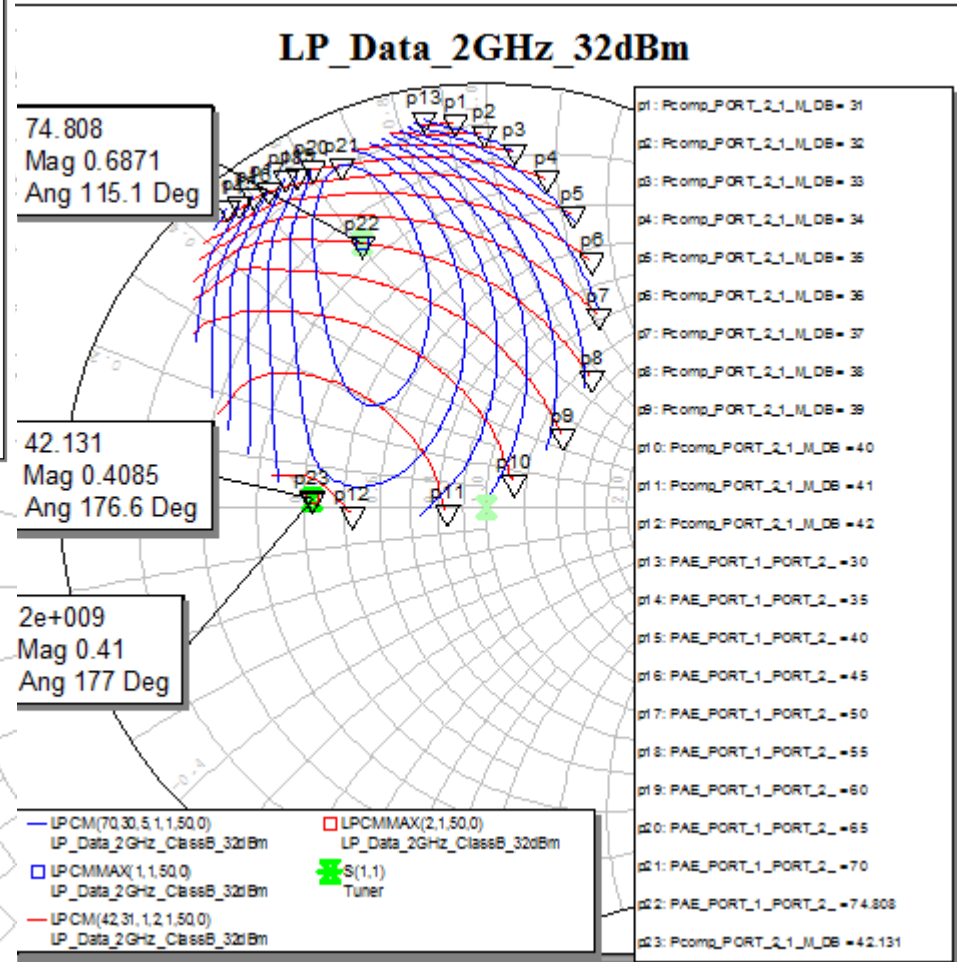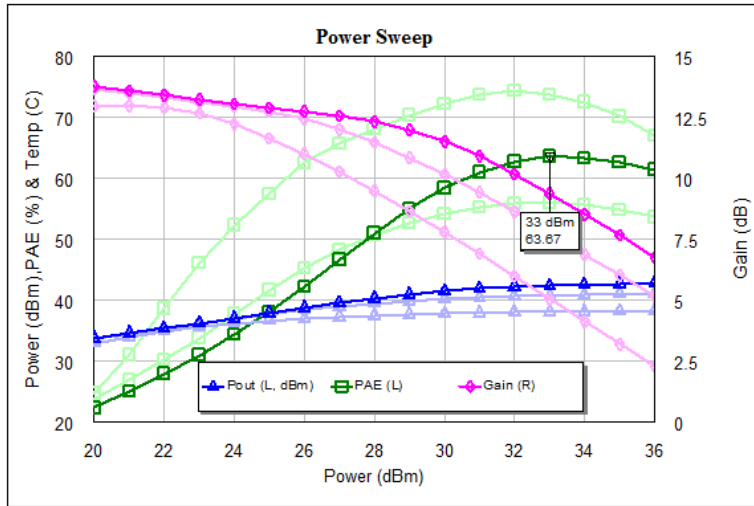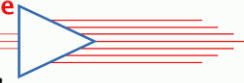


33dBm

# Input Power with Frequency


For wideband designs you have to consider input power vs. frequency. Output power stays ~ constant with frequency.

So, to a first order input power needs to increase at this rate.

Let's take a look →

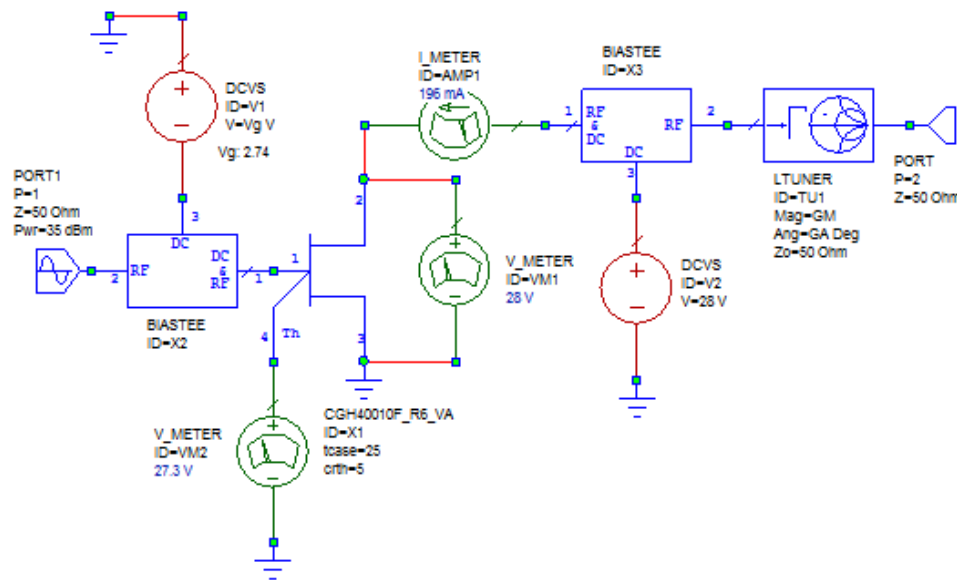


Gain Analysis

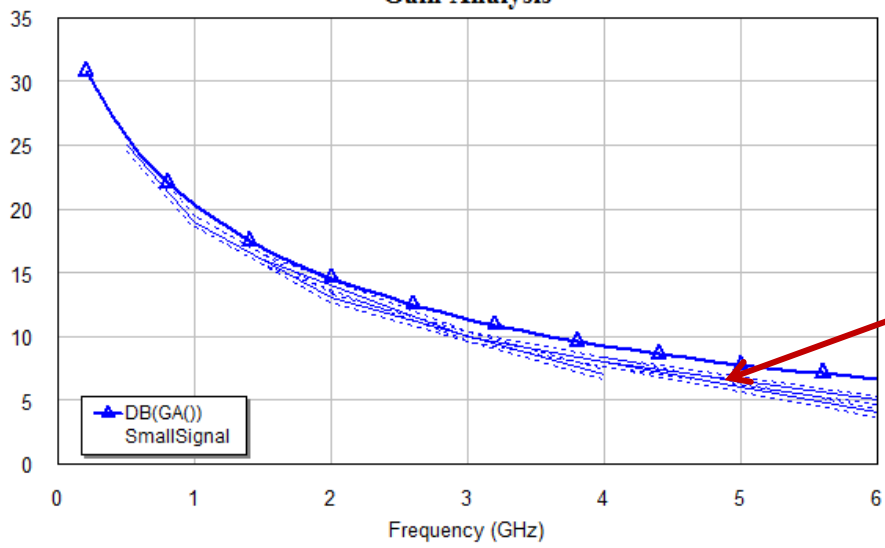

6dB/octave slope



# Input Power with Frequency

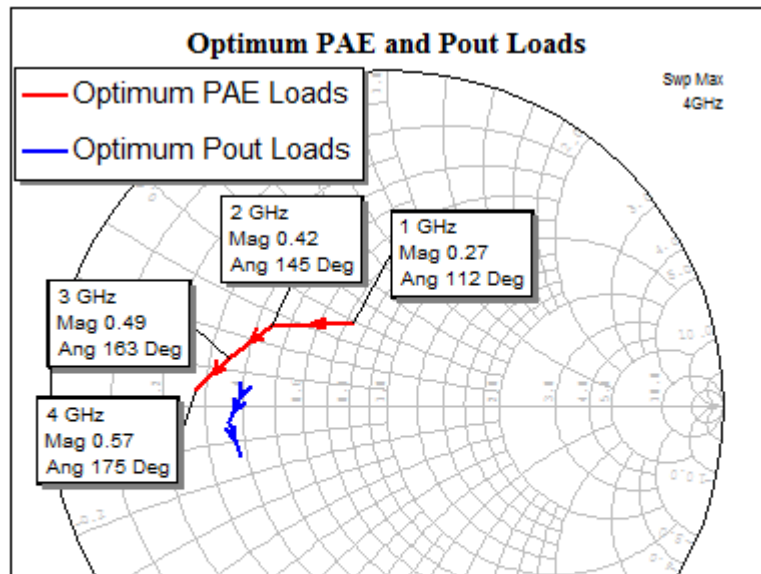


Note:

1. Input power variation for optimum PAE.
2. The maximum Output Power is constant.
3. The intrinsic gain rolls off ~5dB/octave. Output matching recovers some but not all.
4. There is no input matching yet, this shows the need for a positive sloped input power match to achieve the maximum PAE across a wide bandwidth.


Freq. (GHz)	Pin (dBm)	Max. PAE (%)	Load	Pout (dBm)	Gain (dB)	Max. Pout (dBm)	Load
1	28	72	0.27/112°	40.5	12.7	42.5	0.43/174°
2	33	70	0.42/145°	41.4	8.4	42.5	0.44/178°
3	36	69	0.49/163°	41.7	5.7	42.5	0.47/-174°
4	38	67	0.57/175°	41.5	3.5	42.5	0.46/-161°

# Choosing the Optimum Load

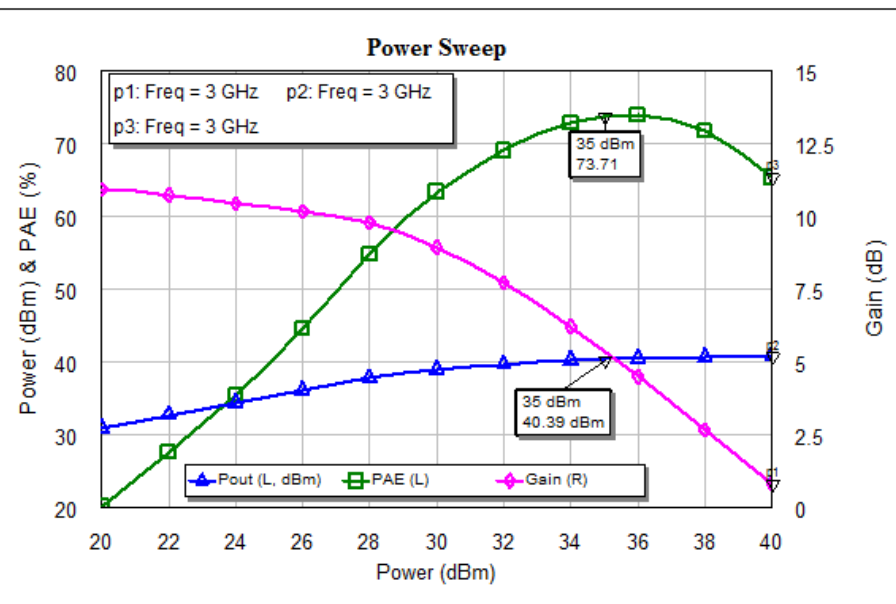


Be aware that the maximum load point may not be the “optimum”

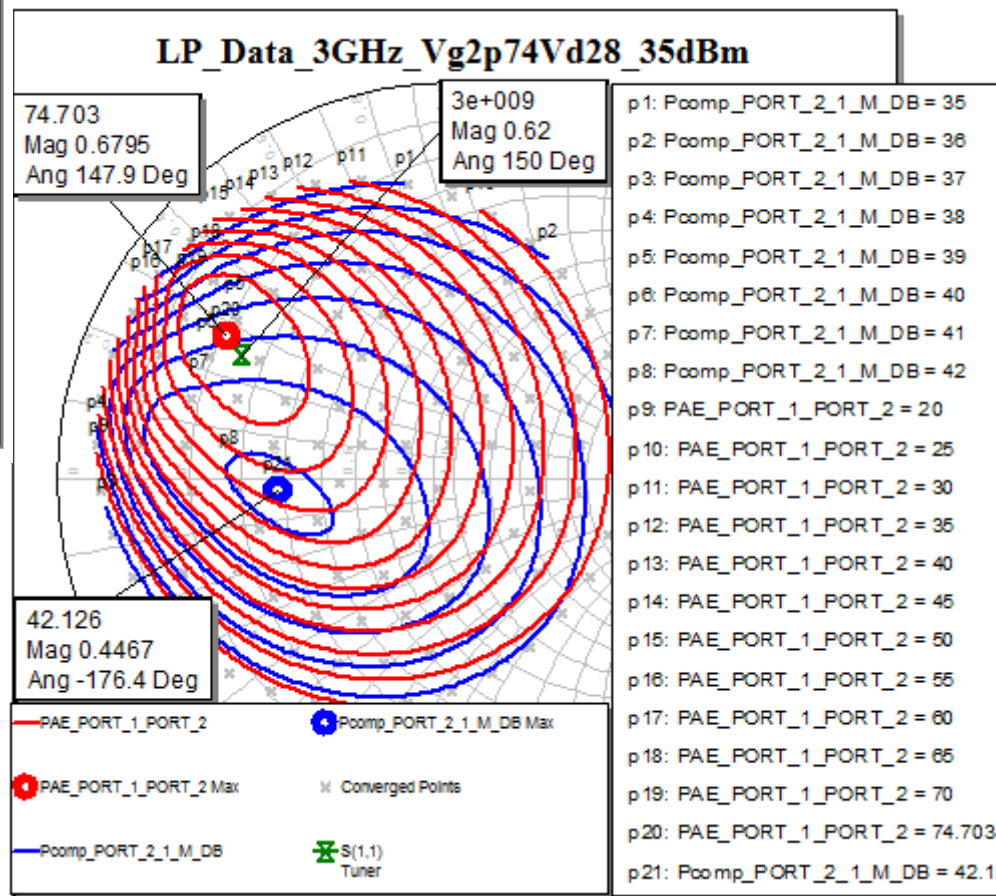Green ‘hour-glass symbol shows load for power sweep.  
By observing swept input power performance as you tune the load you can adjust for the best compromise performance between Power and PAE.




# Returning to the Optimum Loads

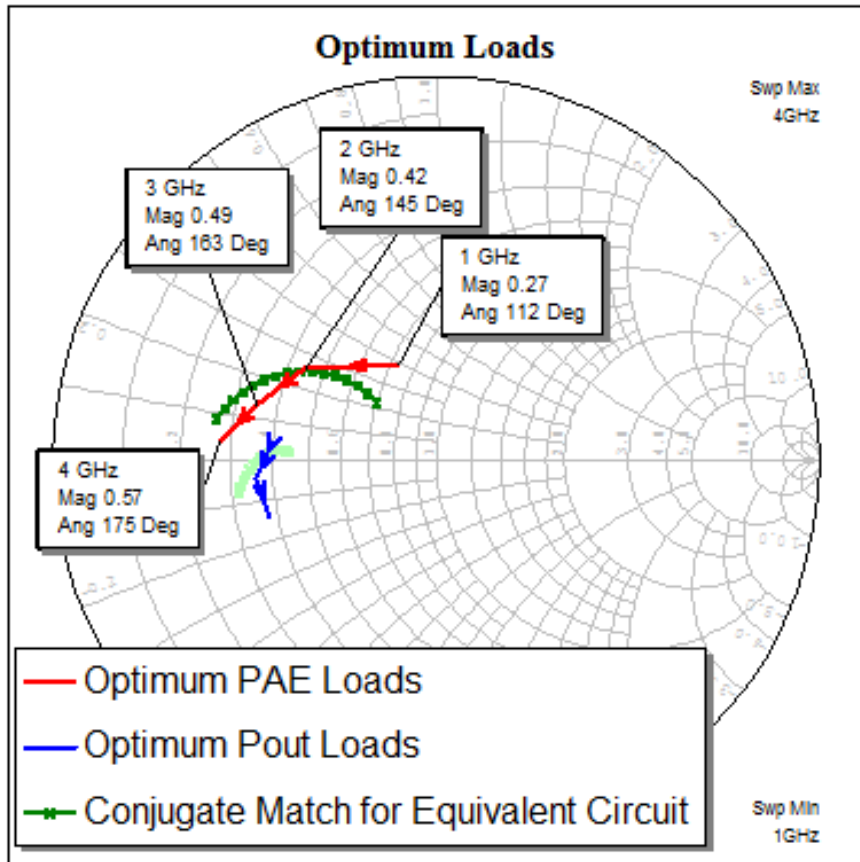


Looking at a simple device output equivalent circuit, including some package de-embedding:

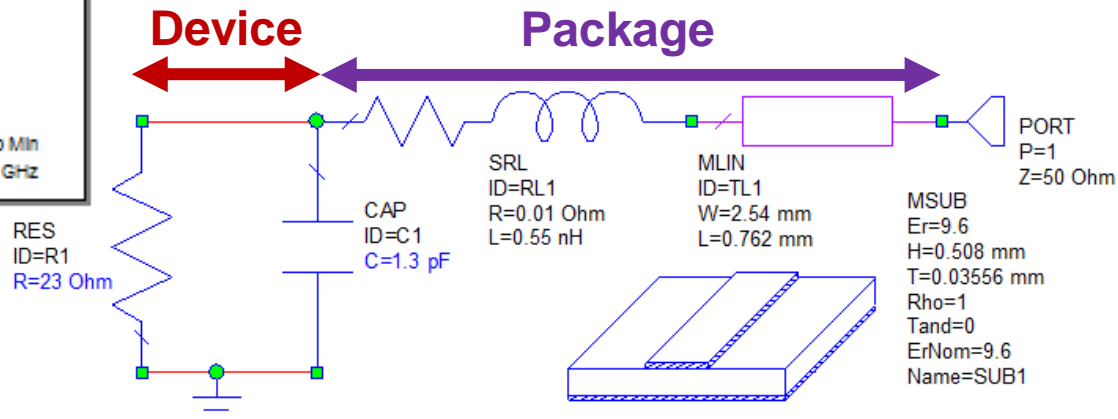The equivalent load resistance increases from  $23\Omega$  for the optimum power loads to  $41\Omega$  for the optimum PAE loads – which agrees with theory 😊





# Load Line Theory

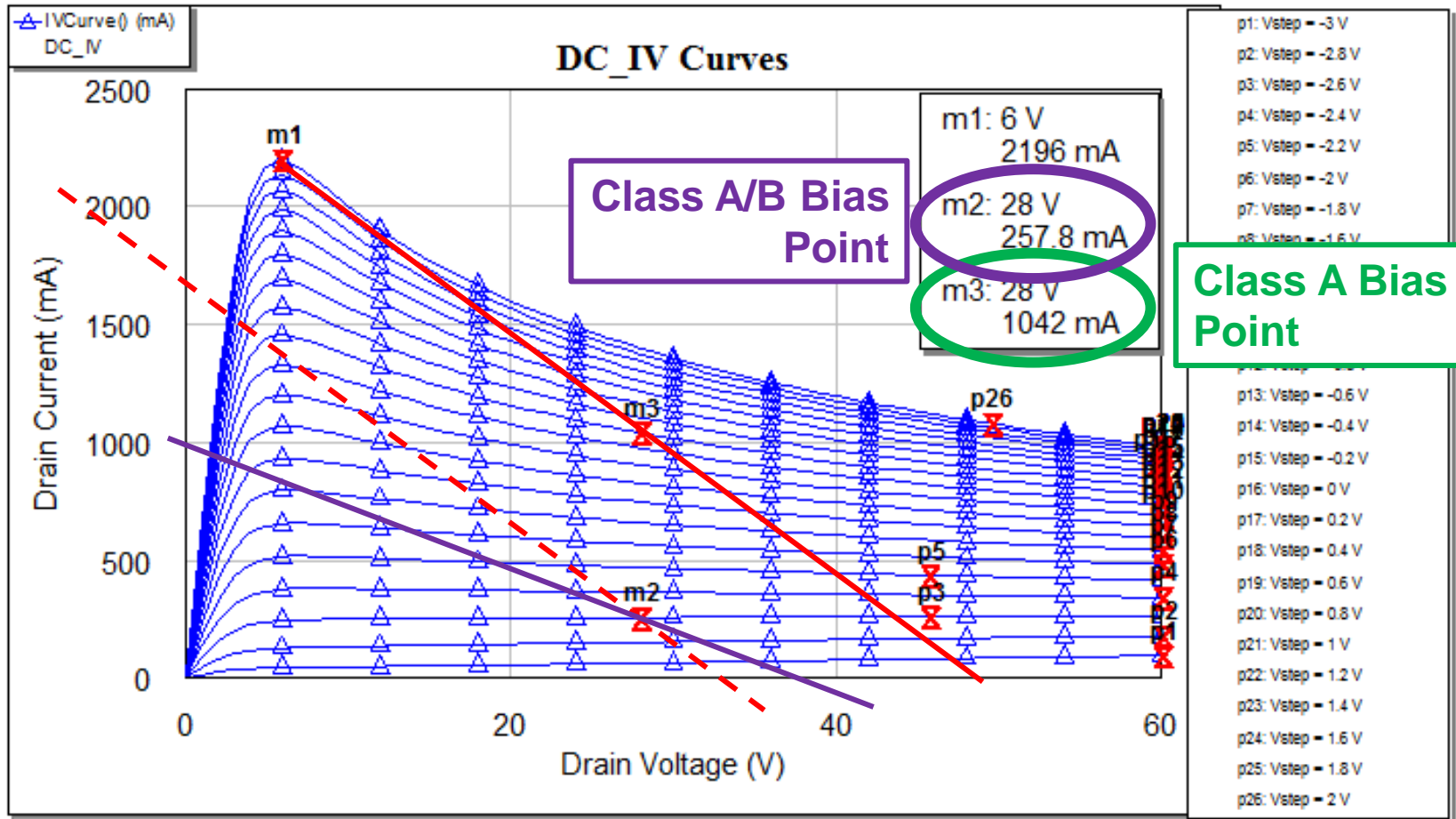

Theory Optimum Power load =  $2x(V_D - V_K) / I_{DS} = 20\Omega$

# Load Line Simulation

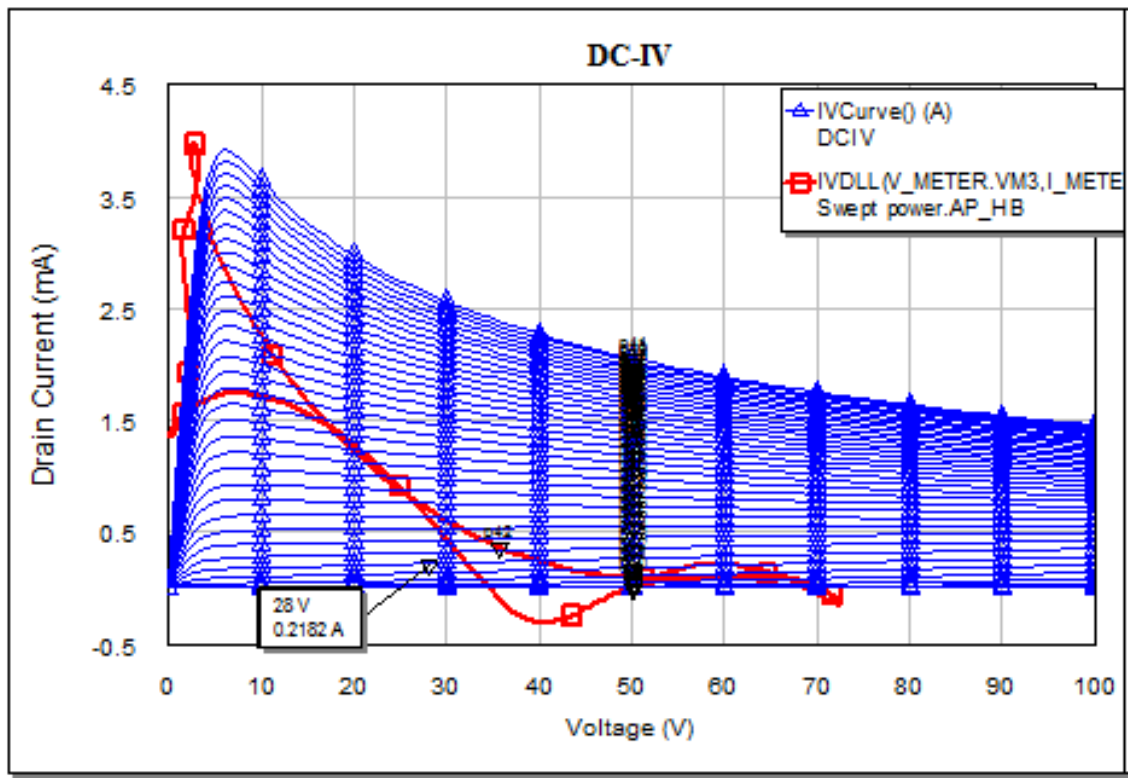
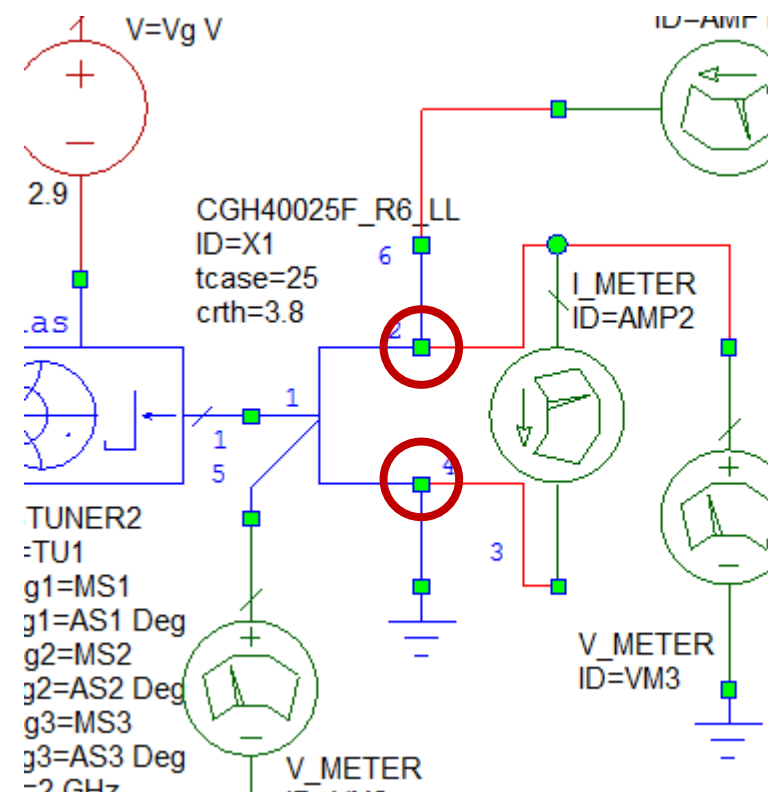


**Addition of internal nodes to model allows direct observation of drain waveforms.**

**As we increase drive Dynamic (RF) load line interacts with limits of the DC-IV envelope.**



# Load Line Simulation

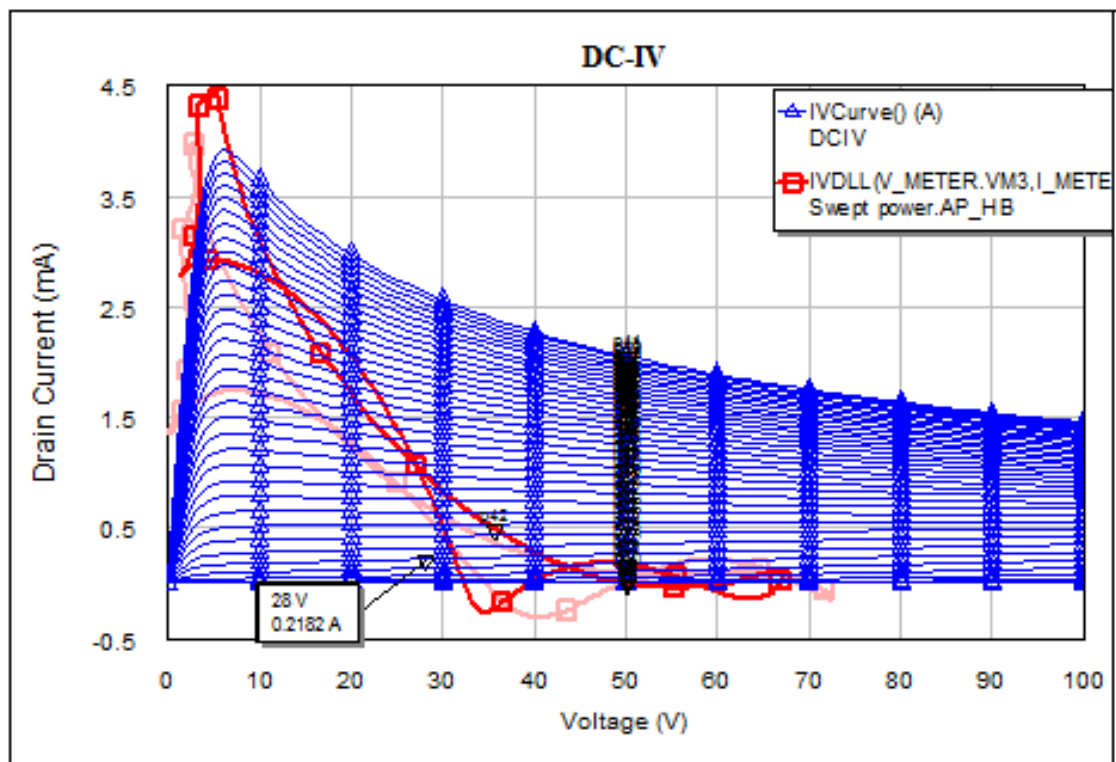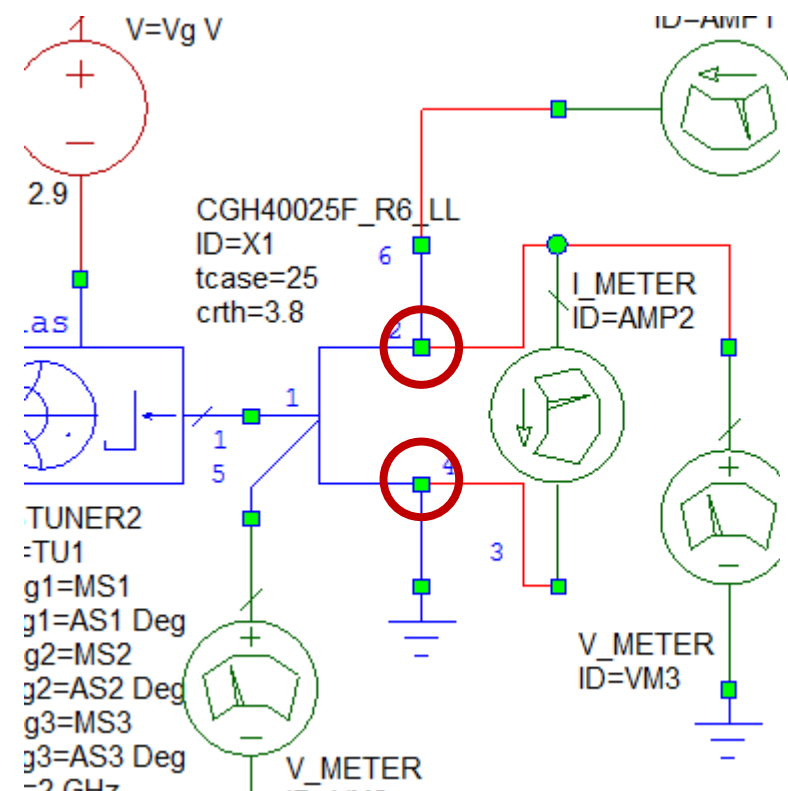


**Addition of internal nodes to model allows direct observation of drain waveforms.**

**Or change load impedance**
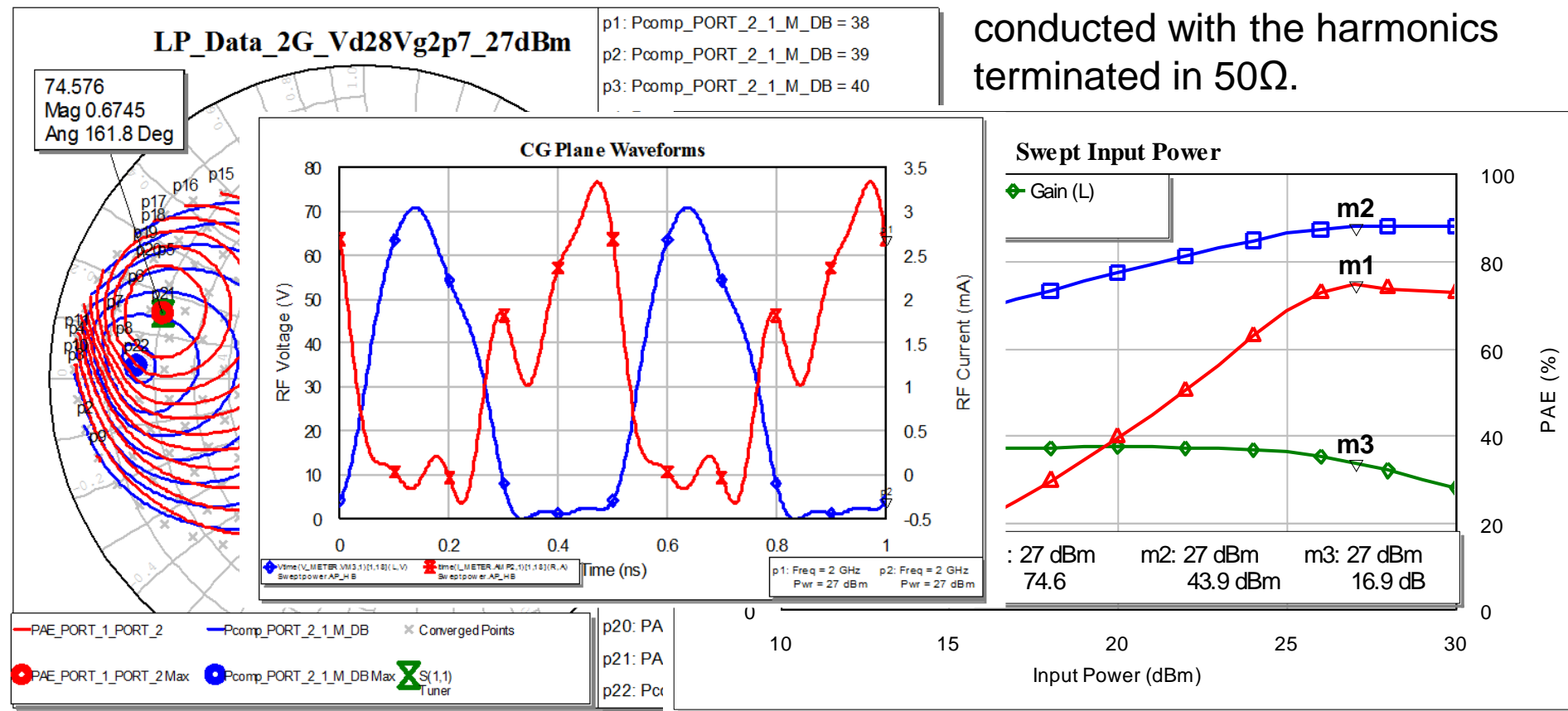
# Harmonic Terminations

A great deal of research has gone into the design of high PAE modes class E, F & J for example, and the importance of harmonic terminations. Using these tools we can see their impact.


Fundamental Load Pull is conducted with the harmonics terminated in 50Ω.


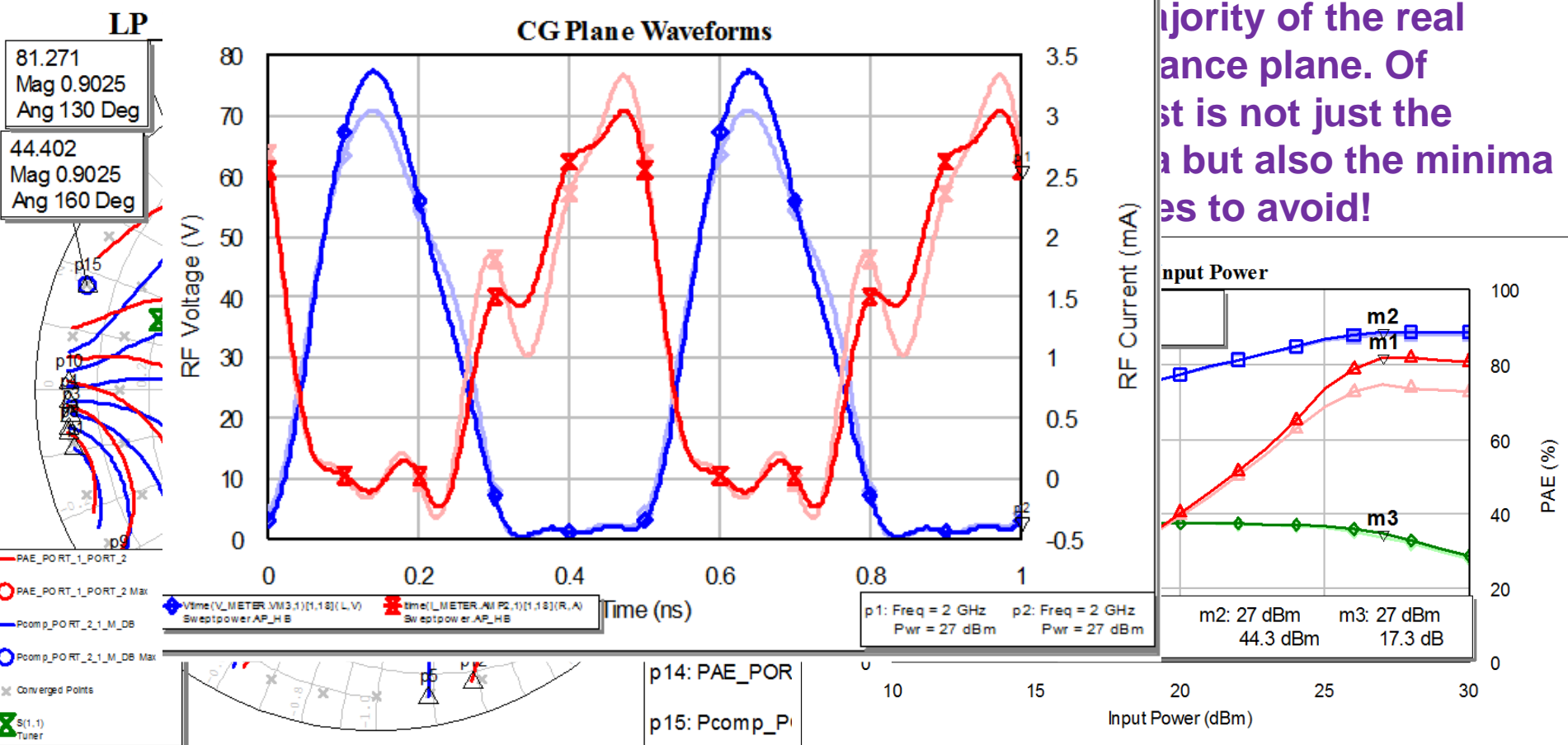
# Harmonic Terminations

Keeping the Fundamental at the optimum PAE impedance a 2<sup>nd</sup> Harmonic Load Pull is conducted with the 3<sup>rd</sup> harmonic terminated in 50Ω.

We are simulating across majority of the real plane. Of st is not just the a but also the minima es to avoid!




# Harmonic Terminations

Keeping the Fundamental & now 2<sup>nd</sup> at their optimum PAE impedances a 3<sup>rd</sup> Harmonic Load Pull is conducted.


We now have almost half

plane where  
imal  
in see

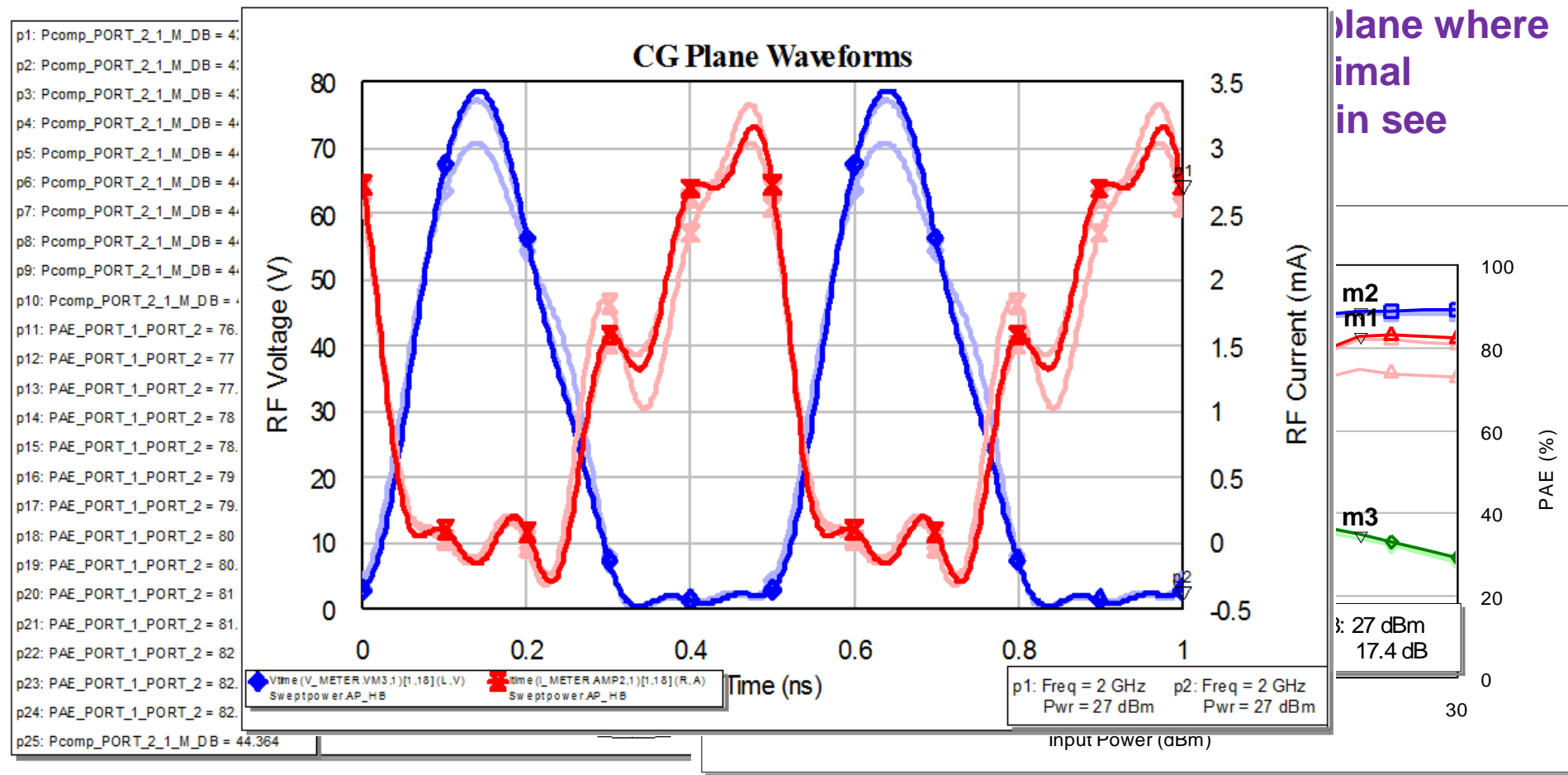
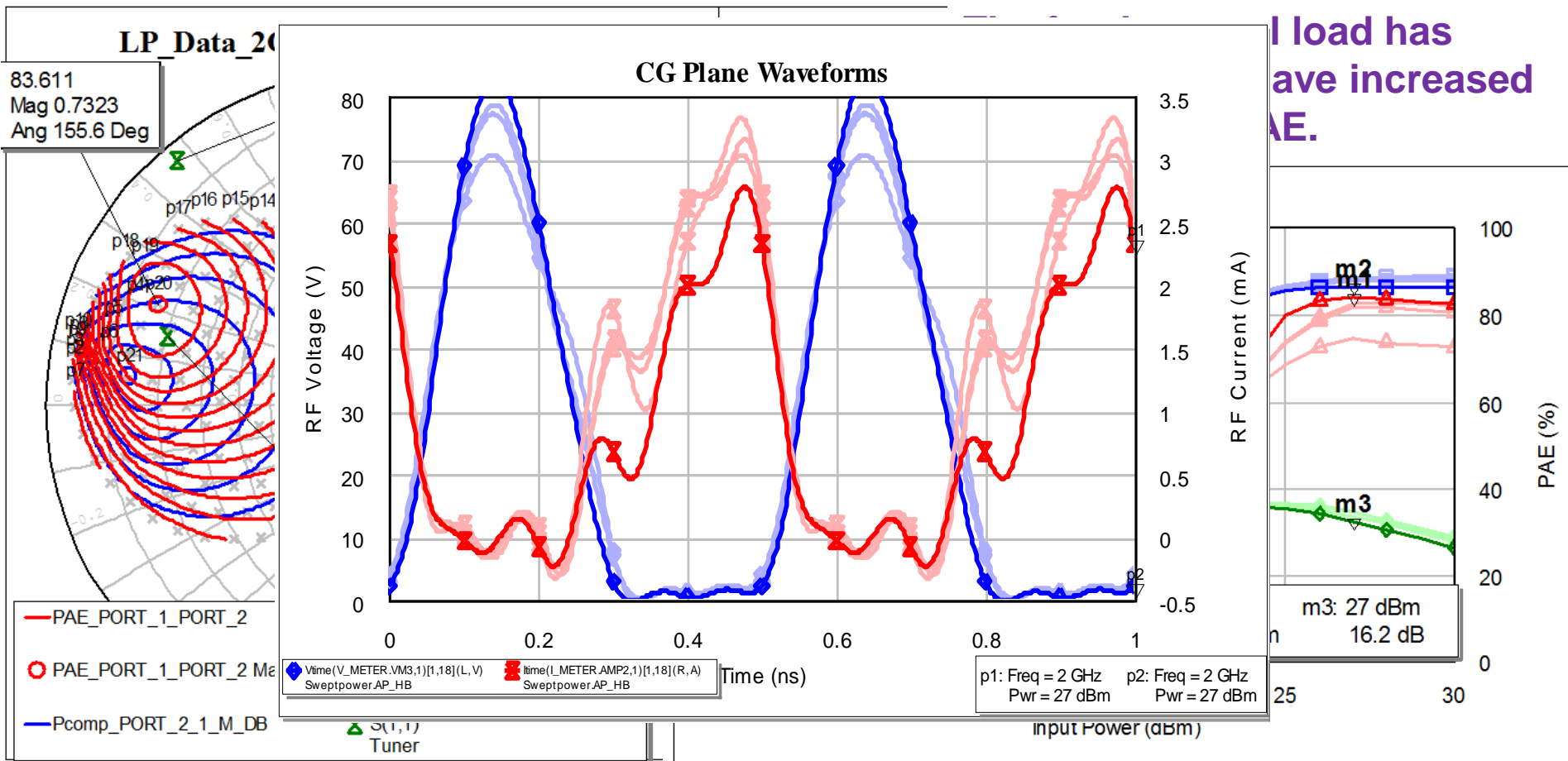
# Harmonic Terminations

Now we have all our terminations optimised, or have we? Re-do the fundamental load pull with the optimum PAE harmonic terminations -




RF load has  
increased  
PAE.




# Harmonic Terminations

LP Data\_2G\_Vd28Vg2p7\_27dBmComparison

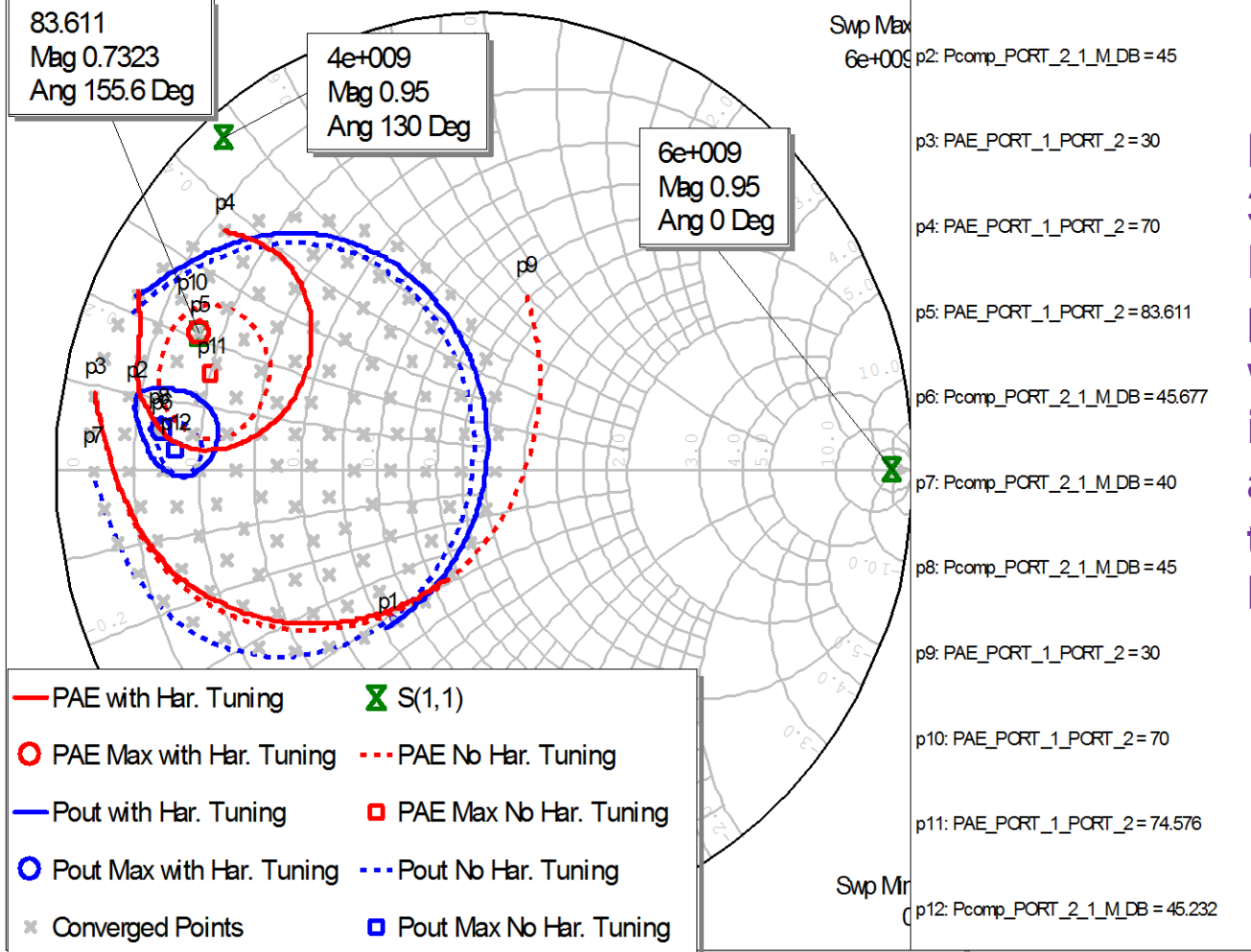

No significant change at 30% PAE and 40dBm Pout, but increase in the peaks and consequently a wider impedance range included in the 70% PAE and 45dBm Pout, indeed these two regions now have a significant overlap.
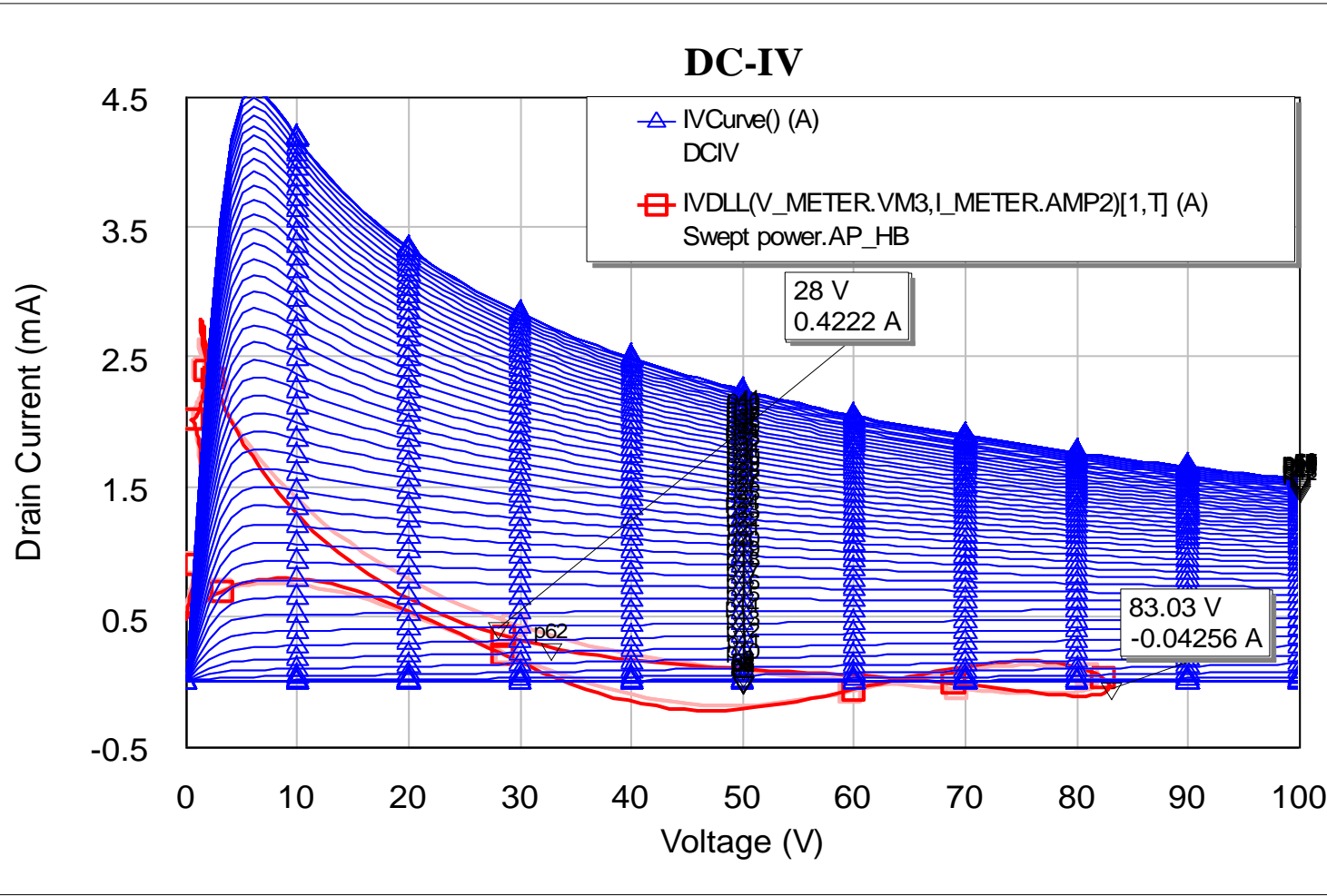
# Dynamic Load Line & Harmonic Terminations



**Notice that we are avoiding high current swings in favour of higher voltage swings.**

**Fundamental, 2<sup>nd</sup>, & 3<sup>rd</sup> Optimum. Note nearly 3x Drain Voltage Swing.**


# Optimum Load Design is a Cyclical Process

## Harmonic Load Pull Steps:

1. Optimum Fundamental Drive Power.
2. Optimum Fundamental Load - Check (1) is still true.
3. 2<sup>nd</sup> Harmonic LP – Check (1) & (2) are still true.
4. 3<sup>rd</sup> Harmonic LP – Check (1), (2) and (3) are still true.
5. Go on to next frequency!

**Remember it is not only about finding the optimums - you also need to know where to avoid!**

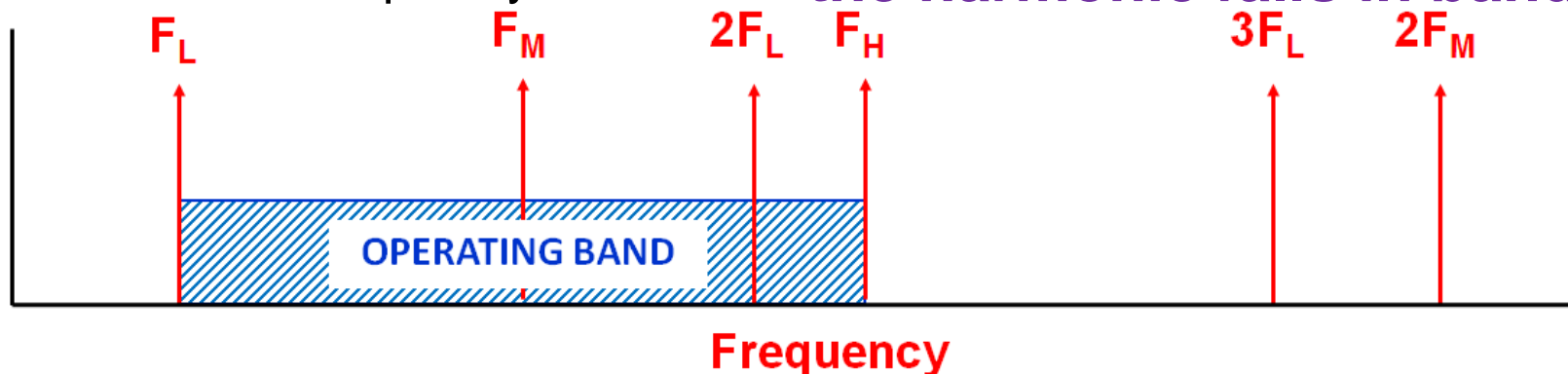**We can't always use the optimum harmonic termination. If we are doing wide bandwidth designs the harmonic falls in band.**




# Broadband Matching:- Insertion Loss and Match

**Load Pull gives the performance before any matching circuit -**

Broadband Matching circuitry seeks to resolve two key problems:

- i. How to maximise bandwidth with a minimum Reflection Coefficient,  $\Gamma$ .
- ii. How to minimise the number of matching elements,  $N$ , for a given bandwidth, (typically loss  $\propto N$ ).

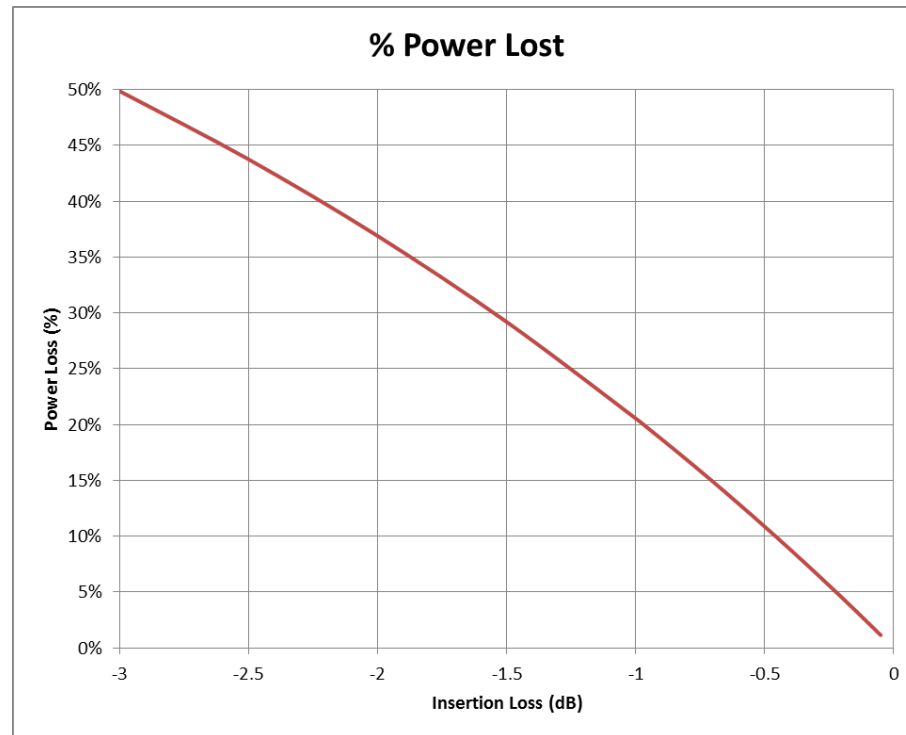
**Don't confuse  $L_T$  with insertion loss that has got to be included too!**



$\Gamma$	0.1	0.18	0.2	0.25	0.35	0.4	0.5	0.71	0.8
RL (dB)	20	15	14	12	9	8	6	3	1.9
$L_T$ (dB)	0.04	0.14	0.18	0.28	0.58	0.76	1.25	3.0	4.44
VSWR	1.22	1.43	1.50	1.67	2.1	2.33	3.00	5.85	9.00



**$\Gamma$ , Return Loss, Mismatch (Transmission) Loss and VSWR.**

# Current Approaches and Performance

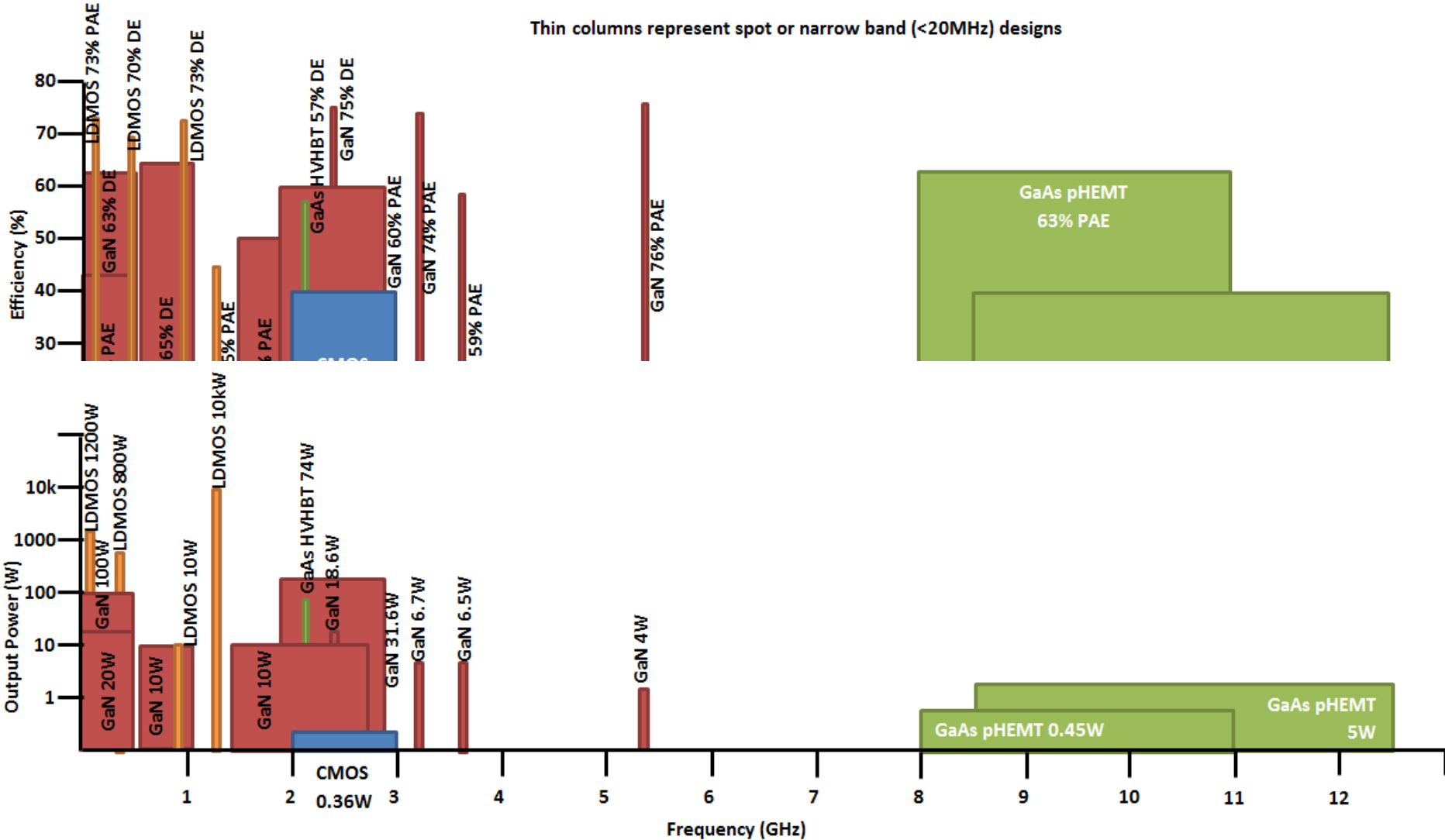



# Current Approaches and Performance

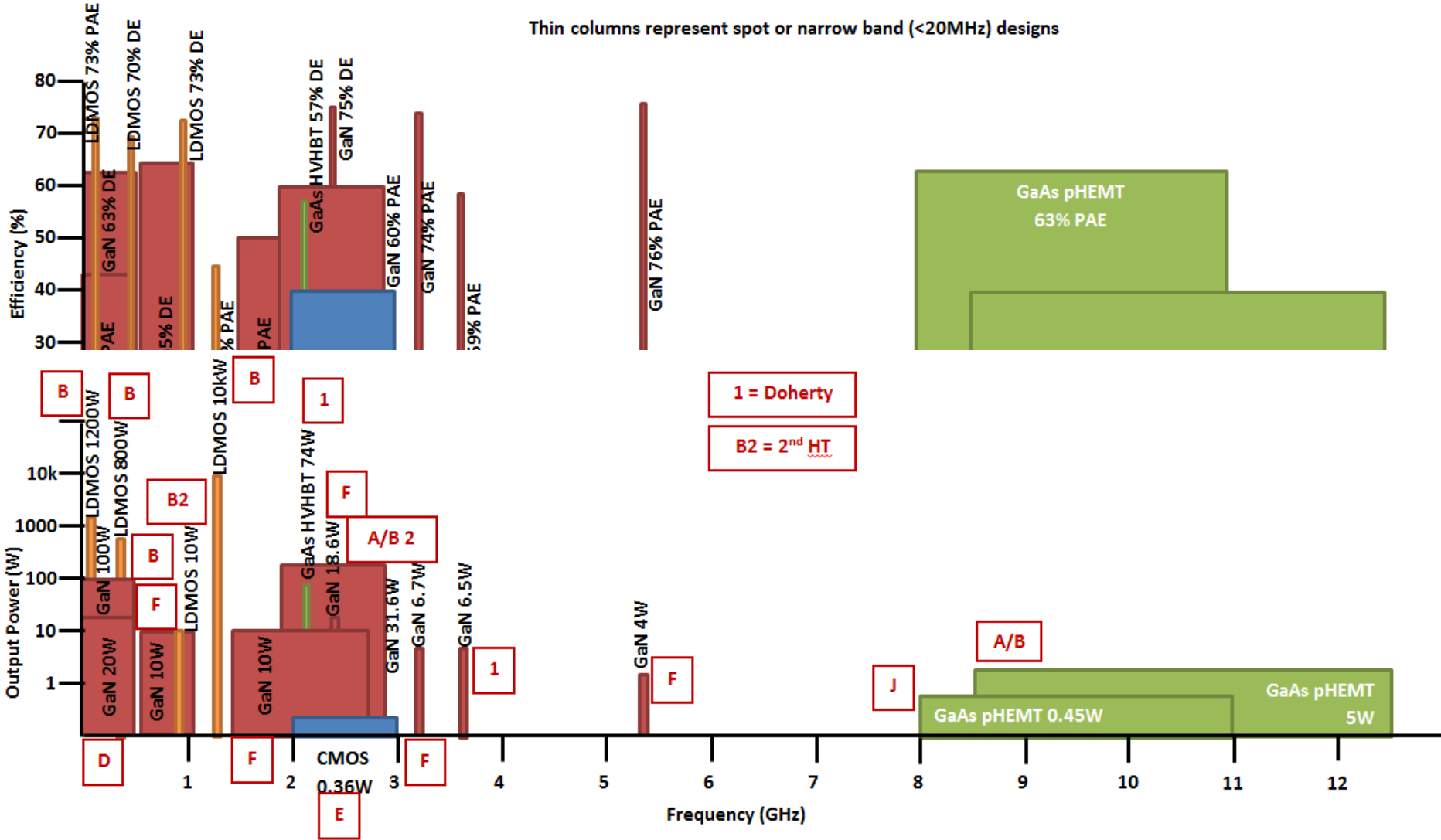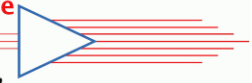

# Current Approaches and Performance



Technology	Class	Fmin GHz	Fmax GHz	Eff. %	Pout	Dev.Power	Year	Reference
cmos	E	2	3	40.2 PAE	0.36	NS	2013	Broadband and High-Efficiency Power Amplifier that Integrates CMOS and IPD Technology
GaAs pHEMT	A/B	8.5	12.5	40 PAE	5	8x 0.8	2013	Design Procedure 4 Hi-Eff and Compact-Size 5–10W MMIC PAs in GaAs pHEMT Tech.
GaN HEMT	F	5.65	5.7	76 PAE	4	0.96mm	2012	Ultra High Efficiency Microwave Power Amplifier for Wireless Power Transmission
GaN HEMT	F-1	3.27	3.3	74 PAE	6.7	10	2010	First-Pass Design of High Efficiency Power Amplifiers using Accurate Large Signal Models
GaN HEMT	F-1 PushPull	2.5	2.55	75 DE	18.6	2x 10	2010	First-Pass Design of High Efficiency Power Amplifiers using Accurate Large Signal Models
GaAs pHEMT	J	8	11	63 DE	0.45	0.6	2011	GaAs X-Band Hi Eff (>65%) Broadband (>30%) Amp MMIC based on Class B to J Continuum
GaAs HVHBT	Doherty	2.1	2.15	57 DE	74	2x 120	2010	Doherty Power Amp using 2nd Gen. HVHBT Technology for Hi Eff Basestation Applications
LDMOS	B 2HT	0.9	0.95	73 DE	10	30	2010	Lumped-element Output Networks for High-efficiency Power Amplifiers
GaN HEMT	B?	0.01	0.5	43 PAE	100	4x 45	2009	Design of a 100Watt High-Efficiency Power Amplifier for the 10-500MHz Band
GaN HEMT	VM D	0.05	0.5	63 DE	20	10 x2	2011	Development of a WB Highly Efficient GaN VoltageModeClassD VHFUHF Power Amplifier
GaN HEMT	Doherty	3.5	3.55	59 PAE	6.5	6 x2	2013	A LinearandEfficientDohertyPAat3p5GHz
GaN HEMT	F	0.55	1.1	65 DE	10	10	2011	A Novel Hi Eff BB Continuous ClassF RFPA Delivering 74% Average Eff for an Octave BW
GaN HEMT	A/B 2HT	1.9	2.9	60 DE	31.6	45	2010	Design of a BB Highly Efficient 45W GaN PA via Simplified Real Freq Technique
GaN HEMT	J	1.4	2.7	50 PAE	10	10	2009	Methodology4RealizingHiEffClassJinaLinearBroadbandPA
LDMOS	B	0.5	0.505	66 PAE	680	1000	2012	Developments of High CW RF PowerSSAatSoleil
LDMOS	B	1.3	1.305	45 PAE	10000	160	2012	1st Experience At Elbe with new 1.3GHz CWRW System Based on 10kWSSA
LDMOS	B	0.085	0.115	73 PAE	1200	1200	2012	Own work

Recommend Cree Website for extensive list of technical papers:

<http://www.cree.com/RF/Document-Library>
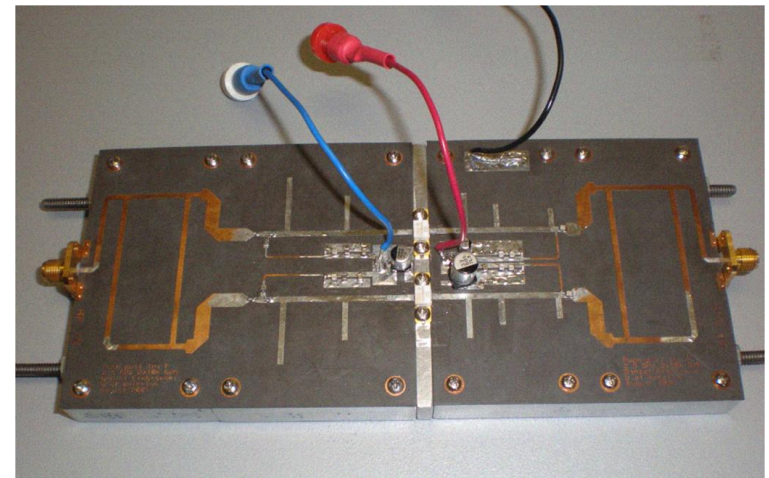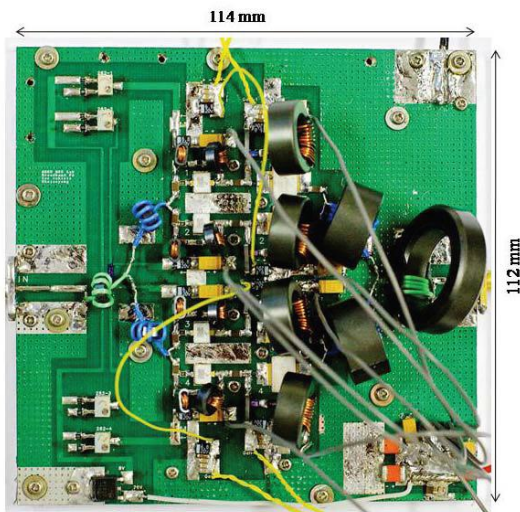
## Balanced Approach:


A number of the papers just referenced used balanced amplifiers to achieve high power and efficiency, particularly the very high power LDMOS. Two GaN exceptions were the broad band “*Design of a 100Watt High-Efficiency Power Amplifier for the 10-500MHz Band*” (left) and the 2.5GHz “*First-Pass Design of High Efficiency Power Amplifiers using Accurate Large Signal Models*” (right). Interesting both use devices capable of 2x the output power they achieve.



# Topology Counts


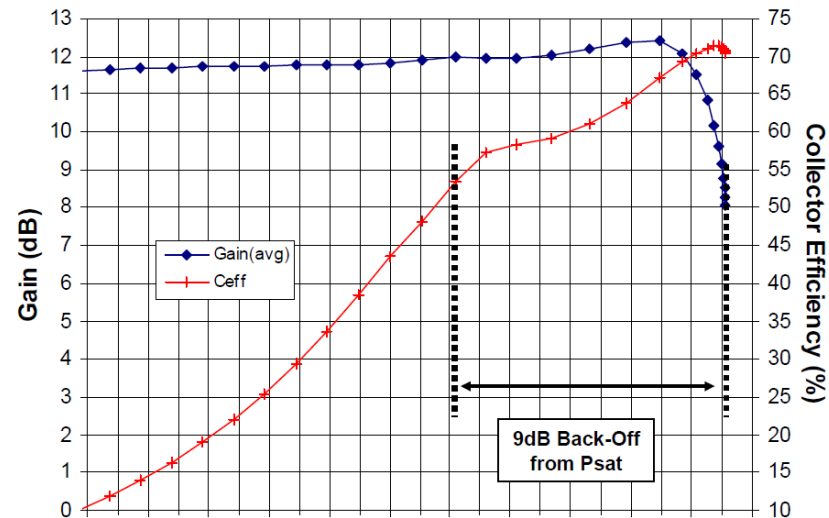
## Doherty Approach:

Uses parallel devices to increase efficiency at back off as graph from “*Doherty Power Amplifiers using 2nd Generation HVHBT Technology for High Efficiency Basestation Applications*”.


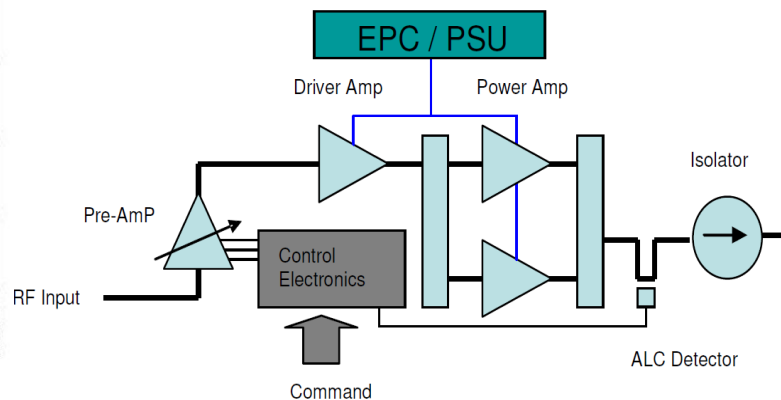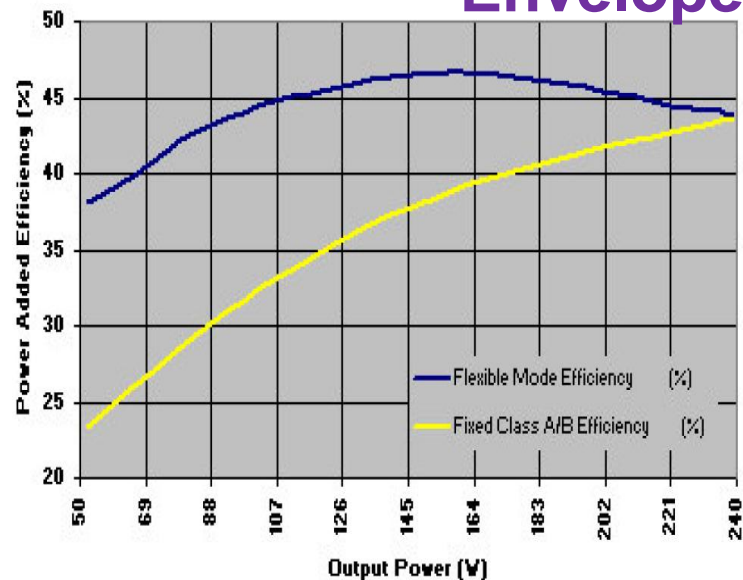
## Envelope Tracking

Astrium 200W GaN demonstrator performance using drain bias adjustment for increased PAE.



# Summary

- a) Device self-heating model.
- b) Input match.
- c) Wide Band designs ‘tapered’ input drive level.
- d) Observe the Current Generator Plane waveforms – 6 port device model.
- e) Don’t forget mismatch and insertion losses of output matching circuit.
- f) Harmonic terminations - they can both enhance and degrade performance.
- g) Models aren’t valid over an infinite range.



# Questions?

## Thank You!

**Sponsored by:**

**[www.awrcorp.com](http://www.awrcorp.com)**

**[www.cree.com](http://www.cree.com)**

**PoweRFul Microwave**

**[www.powerful-microwave.co.uk](http://www.powerful-microwave.co.uk)**